

Cache Design Project

Class: CMPE 413

Semester: Fall 2022

Completed by: Mick Harrigan and Daniel Cleaver

Date: 2022-11-22

Description


This system from the top level chip all the way down uses many different connected parts to achieve the desired results.

The modules contained within this system are listed here as follows:

- State Machine
- Cache Block
- Tag Block
- Valid Chip Enable Generator
- Registers
- Output Enable Controllers
- Muxes
- 5 bit Counter
- 5 bit Comparator
- Hit/Miss Detector

This is further represented below with a deeper hierarchical design here below.

Chip

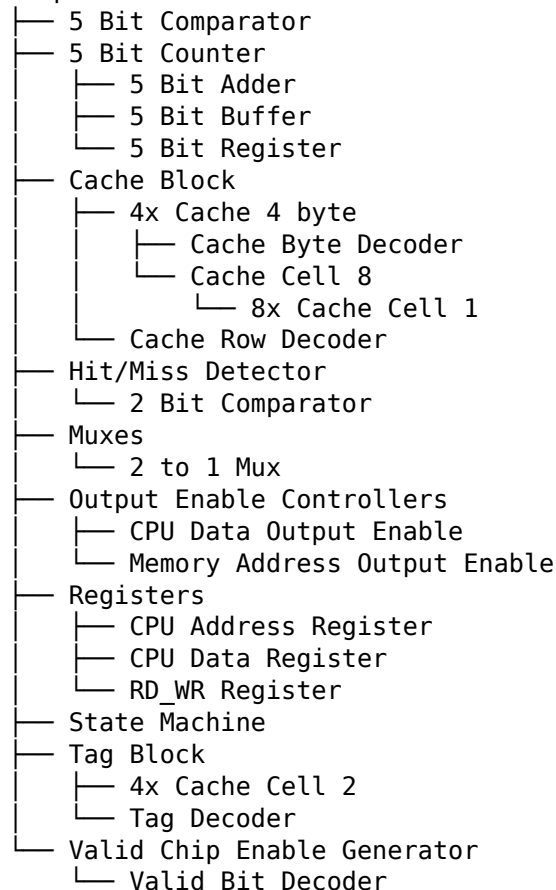

We used github to store files and track changes. Our repo can be found [here](#).

Design Strategy

State Machine

The state machine acts as a controller for all other modules in the top-level chip. The current state is stored in a register, and the output signals are calculated using combinational logic. In addition, the next state is determined based on the current state and the inputs. The behavior of the state machine is described by the following tables.

Table 1 shows the list of states and a description of each.

State name	State Code (Dec)	State Code (Bin)	Action
idle	0	0000	
rd_init	4	0100	Store inputs, read data, check for hit
rd_hit	5	0101	Send data to CPU
rd_miss_mem_ei	12	1100	Send address to Mem
rd_miss_mem_w	13	1101	Wait for Mem
rd_miss_wr	8	1000	Write data to row
rd_miss_rd	6	0110	Read data
rd_miss_send	7	0111	Send data to CPU
wr_init	14	1110	Store inputs, check for hit
wr_hit	9	1001	Write data
wr_miss	15	1111	Do nothing
reset	1	0001	Reset

Table 2 shows the outputs for each state.

Current State	cpu_busy	counter_ce	counter_rst	cpu_data_oe	mem_add_oe	mem_enable	cb_d_wr_control	cb_ce	cb_rd_wr	cb_offset_control	tb_ce	tb_rd_wr	valid_ce	valid_ce_all	valid_rd_wr	valid_d_wr
idle	0	0	0	0	0	0	x	0	x	x	0	x	0	0	x	x
rd_init	1	0	0	0	0	0	x	1	1	0	1	1	1	0	1	x
rd_hit	0	0	0	1	0	0	x	1	1	0	0	x	0	0	x	x
rd_miss_mem_enable	1	1	0	0	1	1	x	0	x	x	0	x	0	0	x	x
rd_miss_mem_wait	1	1	0	0	0	0	x	0	x	x	0	x	0	0	x	x
rd_miss_wr	1	1	0	0	0	0	1	1	0	1	1	0	1	0	0	1
rd_miss_rd	1	0	1	0	0	0	x	1	1	0	0	x	0	0	x	x
rd_miss_send	0	0	0	1	0	0	x	1	1	0	0	x	0	0	x	x
wr_init	1	0	0	0	0	0	x	0	x	x	1	1	1	0	1	x
wr_hit	1	0	0	0	0	0	0	1	0	0	0	x	0	0	x	x
wr_miss	1	0	0	0	0	0	x	0	x	x	0	x	0	0	x	x
reset	0	0	1	0	0	0	x	0	x	x	0	x	x	1	0	0

Table 3 shows the possible state transitions, based on the current state and inputs.

Table 3: State Transition Table

Curr state	Inputs						Next state
	cpu_rd_wm	cpu_start	cpu_reset	count1	count2	hit_miss	
idle	1	1	0				rd_init
idle	0	1	0				wr_init
idle	x	x	1				reset
idle	x	0	0				idle
rd_init			0		0		rd_miss_mem_enable
rd_init			0		1		rd_hit
rd_init			1		x		reset
rd_miss_mem_enable			0				rd_miss_mem_wait
rd_miss_mem_enable			1				reset
rd_miss_mem_wait			0	0			rd_miss_mem_wait
rd_miss_mem_wait			0	1			rd_miss_wr
rd_miss_mem_wait			1	x			reset
rd_miss_wr			0		0		rd_miss_wr
rd_miss_wr			0		1		rd_miss_rd
rd_miss_wr			1		x		reset
rd_miss_rd			0				rd_miss_send
rd_miss_rd			1				reset
rd_miss_send			0				idle
rd_miss_send			1				reset
rd_hit			0				idle
rd_hit			1				reset
wr_init			0		0		wr_miss
wr_init			0		1		wr_hit
wr_init			1		x		reset
wr_miss			0				idle
wr_miss			1				reset
wr_hit			0				idle
wr_hit			1				reset
reset	1	1	0				rd_init
reset	0	1	0				wr_init
reset	x	x	1				reset
reset	x	0	0				idle

1 Bit Cache Cell

The single bit cell is built using a modified DFF, transmission gate, and a specialized decoder. Each of these parts are required for the operation of the cell as it is defined.

The modified DFF is used as the single bit storage system, with a write enable signal as its chip enable and a constant tie low for its reset.

The transmission gate controls whether or not the data bit is being read from or not.

The decoder selects if the cell should be reading or writing, and thus affects the output of the transmission gate and input of the DFF.

4x4 Byte Cache Block

The 4x4 Byte cache block stores all 16 Bytes of data through the use of 4 rows of 4 bytes of 1 bit cache cells.

This top level module for the cache takes the data byte and decodes other input signals to determine a write or read.

The data given to this system is then decoded and passed to the specific row to further parse the data. This is done through passing signals through to lower modules within this top level one.

Once the specified row is chosen that module gets the specific offset to either read or write from where it gets passed down into the specific byte and then cells themselves.

VHDL Code

The source code for the project is located [here](#), in the src directory.

The full contents of every file are also given in Appendix 1.

Simulations

The following sections include waveforms for the major components of the cache. For each one, we used the top level testbench provided by the TA and Professor. This test shows full functionality of the design and includes each of the four major scenarios (read miss, read hit, write miss, write hit). To test the state machine and cache block, we replaced the chip's signals with signals specific to that module.

The testbench vhd file and input and output text files are located [here](#). The contents of these files are also shown in Appendix 2.

Chip

Figure 1 shows the waveforms for the top-level chip. These results match the pdf that was provided near the beginning of the project.

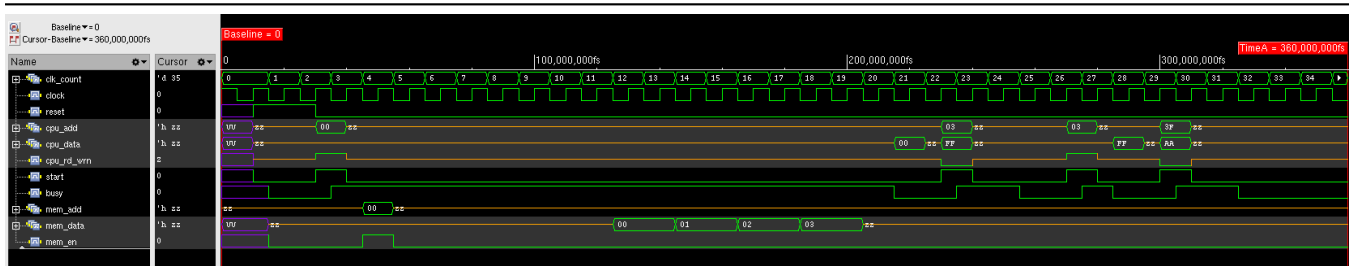


Figure 1: Testbench Waveforms for Chip

State Machine

Figure 2 shows the waveforms for the state machine. All the inputs and outputs are shown, along with the current state.

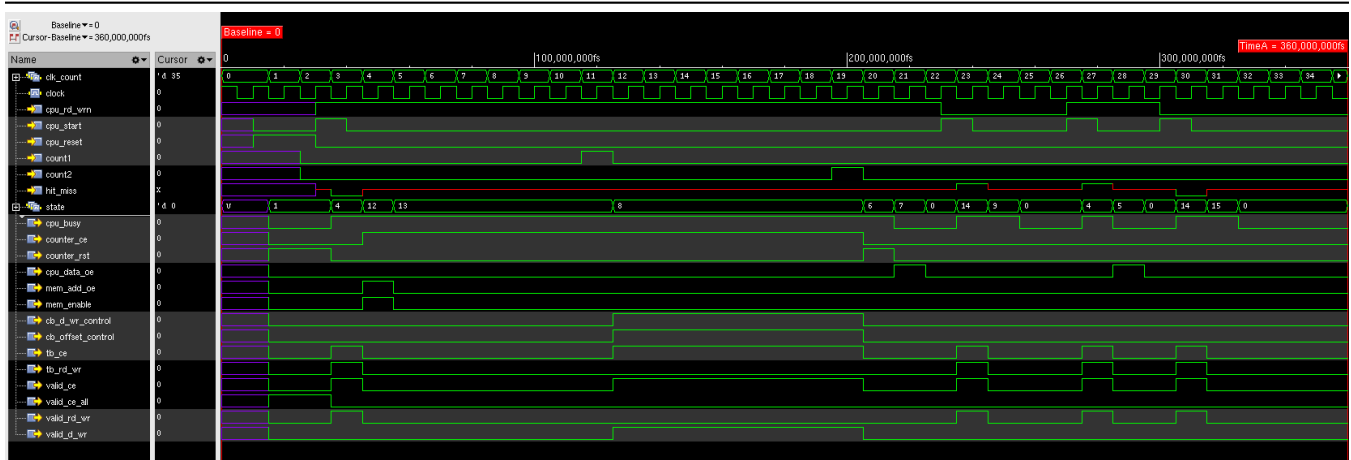


Figure 2: Testbench Waveforms for State Machine

Cache Block

Figure 3 shows the waveforms for the cache block. This shows what happens when the cache is written to or read from.

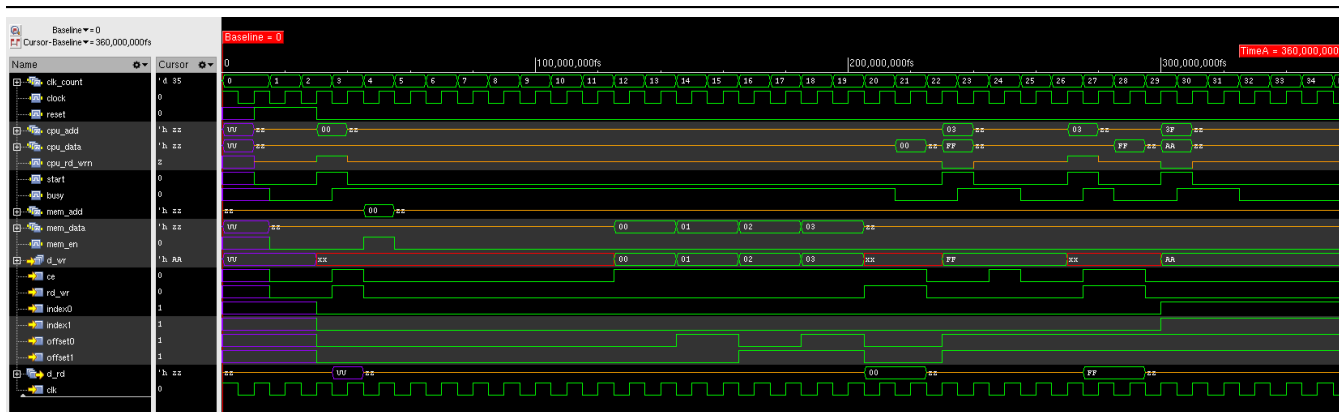


Figure 3: Testbench Waveforms for Cache Block

Work Breakdown

Breakdown of commits to the repo are listed [here](#). This is a chronicle of all changes and updates that each person did over the course of the development of this project. Looking deeper into the commit history shows a list of all changes that were pushed to the repo and from which user. Clicking on any of the commits will show which files were changed, added, removed, or moved.

In terms of lines written by each person, more were written in Dan's commits due to his dealing with longer files, whereas Mick spent more time on creating more smaller low-level files that were used throughout the project. The overall amount of code used in the final version of this VHDL library is fairly even with a similarly even split of the workload. Lastly, writing of the documentation for the project was done simultaneously by both team members through the use of live coding.

Moving forward, the plan for the layouts is to split up time on the primitives and then each work with the modules that we are most familiar with. This should result in an even time spent on the layouts as well as the VHDL.

Conclusion

This project has taught many different skills and tools to be used later in both of our careers. From learning more simple things such as Git and software control structures, to more specific to this class with VHDL and hierarchical design. We expect this to continue with the second half of the project with creating the layouts of the files and systems we designed to eventually have a fully functional cache system.

With all of this in mind this project has been a success in both learning and applying the topics learned in class as well as applicable to our careers as we prepare for our time after graduation.

Appendix 1: VHDL Source Code

```
-- File: chip.vhd
-- Top level cache

library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity chip is
  port(
    cpu_add      : in  std_logic_vector(5 downto 0);
    cpu_data     : inout std_logic_vector(7 downto 0);
    cpu_rd_wrn   : in  std_logic;
    start        : in  std_logic;
    clk          : in  std_logic;
    reset        : in  std_logic;
    mem_data     : in  std_logic_vector(7 downto 0);
    Vdd          : in  std_logic;
    Gnd          : in  std_logic;
    busy         : out std_logic;
    mem_en       : out std_logic;
    mem_add      : out std_logic_vector(5 downto 0)
  );
end chip;

architecture structural of chip is
  component tie_low
    port(
      output: out std_logic
    );
  end component;

  component tie_high
    port(
      output: out std_logic
    );
  end component;

  -- state machine
  component statemachine
    port(
      clk          : in std_logic;

      -- Inputs
      cpu_rd_wrn   : in std_logic;
      cpu_start    : in std_logic;
      cpu_reset    : in std_logic;

      count1       : in std_logic;
      count2       : in std_logic;

      hit_miss     : in std_logic;

      -- Outputs
      cpu_busy     : out std_logic;
    );
  end component;
end structural;
```

```

        counter_ce      : out std_logic;
        counter_rst     : out std_logic;

        cpu_data_oe     : out std_logic;
        mem_add_oe      : out std_logic;

        mem_enable      : out std_logic;

        cb_d_wr_control : out std_logic;

        cb_ce           : out std_logic;
        cb_rd_wr        : out std_logic;

        cb_offset_control : out std_logic;

        tb_ce           : out std_logic;
        tb_rd_wr        : out std_logic;

        valid_ce        : out std_logic;
        valid_ce_all    : out std_logic;

        valid_rd_wr     : out std_logic;
        valid_d_wr      : out std_logic;
    );
end component;

-- cache block
component cache_block
    port(
        d_wr      : in std_logic_vector(7 downto 0);
        ce        : in std_logic;
        rd_wr     : in std_logic;
        index0    : in std_logic;
        index1    : in std_logic;
        offset0   : in std_logic;
        offset1   : in std_logic;
        d_rd      : out std_logic_vector(7 downto 0);
        clk       : in std_logic;
    );
end component;

-- tag block
component tag_block
    port(
        d_wr      : in std_logic_vector(1 downto 0);
        ce        : in std_logic;
        rd_wr     : in std_logic;
        index0    : in std_logic;
        index1    : in std_logic;
        d_rd      : out std_logic_vector(1 downto 0);
        clk       : in std_logic;
    );
end component;

-- "valid" (4 cells of cache)
component cache_cell1
    port(
        d_wr      : in std_logic;
        ce        : in std_logic;

```

```

        rd_wr    : in std_logic;
        d_rd     : out std_logic;
        clk      : in std_logic
    );
end component;

component valid_ce_gen
    port(
        index0:      in std_logic;
        index1:      in std_logic;
        valid_ce:     in std_logic;
        valid_ce_all: in std_logic;
        valid_ce0:    out std_logic;
        valid_ce1:    out std_logic;
        valid_ce2:    out std_logic;
        valid_ce3:    out std_logic
    );
end component;

component Dlatch
    port ( d    : in  std_logic;
           clk  : in  std_logic;
           q    : out std_logic;
           qbar: out std_logic);
end component;

component dlatch6
    port(
        d      : in std_logic_vector(5 downto 0);
        clk    : in std_logic;
        q      : out std_logic_vector(5 downto 0);
        qbar   : out std_logic_vector(5 downto 0)
    );
end component;

component dlatch8
    port(
        d      : in std_logic_vector(7 downto 0);
        clk    : in std_logic;
        q      : out std_logic_vector(7 downto 0);
        qbar   : out std_logic_vector(7 downto 0)
    );
end component;

component mux2
    port(
        input0  : in std_logic;
        input1  : in std_logic;
        s       : in std_logic;
        output  : out std_logic
    );
end component;

component bus_creator2
    port(
        input1  : in std_logic;
        input0  : in std_logic;

```



```

        output  : out std_logic_vector(1 downto 0)
    );
end component;

component bus_creator6
    port(
        input5   : in std_logic;
        input4   : in std_logic;
        input3   : in std_logic;
        input2   : in std_logic;
        input1   : in std_logic;
        input0   : in std_logic;
        output    : out std_logic_vector(5 downto 0)
    );
end component;

-- oe_d
component output_enable8
    port(
        input     : in std_logic_vector(7 downto 0);
        oe        : in std_logic;
        output     : out std_logic_vector(7 downto 0)
    );
end component;

-- oe_a
component output_enable6
    port(
        input     : in std_logic_vector(5 downto 0);
        oe        : in std_logic;
        output     : out std_logic_vector(5 downto 0)
    );
end component;

-- counter
component counter5
    port(
        clk : in std_logic;
        ce  : in std_logic;
        rst : in std_logic;
        q   : out std_logic_vector(4 downto 0)
    );
end component;

component comparator5s
    port(
        input1      : in std_logic_vector(4 downto 0);
        input2_0    : in std_logic;
        input2_1    : in std_logic;
        input2_2    : in std_logic;
        input2_3    : in std_logic;
        input2_4    : in std_logic;
        output      : out std_logic
    );
end component;

-- hit miss detector
component hit_miss_detector
    port(
        input1 : in std_logic_vector(1 downto 0);

```

```

        input2  : in std_logic_vector(1 downto 0);
        valid   : in std_logic;
        output  : out std_logic
    );
end component;

for tie_low_0: tie_low use entity work.tie_low(structural);

for tie_high_0: tie_high use entity work.tie_high(structural);

for latch_cpu_add: dlatch6 use entity work.dlatch6(structural);

for latch_cpu_data: dlatch8 use entity work.dlatch8(structural);

for latch_cpu_rd_wrn: Dlatch use entity work.Dlatch(structural);

for sm: statemachine use entity work.statemachine(structural);

for counter: counter5 use entity work.counter5(structural);

for comp_0, comp_1: comparator5s use entity work.comparator5s(structural);

for mux2_0, mux2_1, mux2_2, mux2_3, mux2_4, mux2_5, mux2_6, mux2_7, mux2_8,
    mux2_9
    : mux2 use entity work.mux2(structural);

for cb: cache_block use entity work.cache_block(structural);

for bus_creator2_tb_d_wr, bus_creator2_hm_tag: bus_creator2 use entity work.bus_creator2(structural);

for tb: tag_block use entity work.tag_block(structural);

for valid_ce_gen_0: valid_ce_gen use entity work.valid_ce_gen(structural);

for valid0, valid1, valid2, valid3
    : cache_cell1 use entity work.cache_cell1(structural);

for hm: hit_miss_detector use entity work.hit_miss_detector(structural);

for oe_cpu_data: output_enable8 use entity work.output_enable8(structural);

for bus_creator6_mem_add: bus_creator6 use entity work.bus_creator6(structural);

for oe_mem_add: output_enable6 use entity work.output_enable6(structural);

signal b0, b1: std_logic;

signal cpu_add_stored: std_logic_vector(5 downto 0);
signal cpu_rd_wrn_stored: std_logic;
signal cpu_data_stored: std_logic_vector(7 downto 0);

signal counter_ce, counter_rst: std_logic;
signal counter_q: std_logic_vector(4 downto 0);

signal count_to_7, count_to_15: std_logic;

```

```

signal cb_d_wr_control: std_logic;
signal cb_d_wr: std_logic_vector(7 downto 0);
signal cb_offset_control, cb_offset0, cb_offset1: std_logic;
signal cb_ce, cb_rd_wr: std_logic;
signal cb_d_rd: std_logic_vector(7 downto 0);

signal tb_ce, tb_rd_wr: std_logic;
signal tb_d_wr, tb_d_rd: std_logic_vector(1 downto 0);

signal valid_ce, valid_ce_all, valid_rd_wr, valid_d_wr, valid_d_rd: std_logic;
signal valid_ce0, valid_ce1, valid_ce2, valid_ce3: std_logic;

signal hit_miss: std_logic;
signal hm_tag: std_logic_vector(1 downto 0);

signal mem_add_out: std_logic_vector(5 downto 0);
signal cpu_data_oe, mem_add_oe: std_logic;

begin
    tie_low_0: tie_low port map(b0);
    tie_high_0: tie_high port map(b1);

    latch_cpu_add: dlatch6 port map(cpu_add, start, cpu_add_stored, open);

    latch_cpu_rd_wrn: Dlatch port map(cpu_rd_wrn, start, cpu_rd_wrn_stored, open);

    latch_cpu_data: dlatch8 port map(cpu_data, start, cpu_data_stored, open);

    sm: statemachine port map(
        clk,
        cpu_rd_wrn_stored, start, reset,
        count_to_7, count_to_15,
        hit_miss,
        busy,
        counter_ce, counter_rst,
        cpu_data_oe, mem_add_oe,
        mem_en,
        cb_d_wr_control,
        cb_ce, cb_rd_wr,
        cb_offset_control,
        tb_ce, tb_rd_wr,
        valid_ce, valid_ce_all,
        valid_rd_wr, valid_d_wr
    );

    counter: counter5 port map(clk, counter_ce, counter_rst, counter_q);
    -- compare counter5 to 2 values (7 and 15)
    comp_0: comparator5s port map(counter_q, b1, b1, b1, b0, b0, count_to_7);
    comp_1: comparator5s port map(counter_q, b1, b1, b1, b1, b0, count_to_15);

    -- Select the data given to the cache
    mux2_0: mux2 port map(cpu_data_stored(0), mem_data(0), cb_d_wr_control, cb_d_wr(0));
    mux2_1: mux2 port map(cpu_data_stored(1), mem_data(1), cb_d_wr_control, cb_d_wr(1));
    mux2_2: mux2 port map(cpu_data_stored(2), mem_data(2), cb_d_wr_control, cb_d_wr(2));
    mux2_3: mux2 port map(cpu_data_stored(3), mem_data(3), cb_d_wr_control, cb_d_wr(3));
    mux2_4: mux2 port map(cpu_data_stored(4), mem_data(4), cb_d_wr_control, cb_d_wr(4));
    mux2_5: mux2 port map(cpu_data_stored(5), mem_data(5), cb_d_wr_control, cb_d_wr(5));

```

```

mux2_6: mux2 port map(cpu_data_stored(6), mem_data(6), cb_d_wr_control, cb_d_wr(6));
mux2_7: mux2 port map(cpu_data_stored(7), mem_data(7), cb_d_wr_control, cb_d_wr(7));

-- Select the offset given to the cache
mux2_8: mux2 port map(cpu_add_stored(0), counter_q(1), cb_offset_control, cb_offset0);
mux2_9: mux2 port map(cpu_add_stored(1), counter_q(2), cb_offset_control, cb_offset1);

cb: cache_block port map(
    cb_d_wr, cb_ce, cb_rd_wr,
    cpu_add_stored(2), cpu_add_stored(3), cb_offset0, cb_offset1,
    cb_d_rd, clk
);

bus_creator2_tb_d_wr: bus_creator2 port map(cpu_add_stored(5), cpu_add_stored(4), tb_d_wr);
tb: tag_block port map(tb_d_wr, tb_ce, tb_rd_wr, cpu_add_stored(2), cpu_add_stored(3), tb_d_rd, clk);

valid_ce_gen_0: valid_ce_gen port map(
    cpu_add_stored(2), cpu_add_stored(3),
    valid_ce, valid_ce_all,
    valid_ce0, valid_ce1, valid_ce2, valid_ce3
);
valid0: cache_cell1 port map(valid_d_wr, valid_ce0, valid_rd_wr, valid_d_rd, clk);
valid1: cache_cell1 port map(valid_d_wr, valid_ce1, valid_rd_wr, valid_d_rd, clk);
valid2: cache_cell1 port map(valid_d_wr, valid_ce2, valid_rd_wr, valid_d_rd, clk);
valid3: cache_cell1 port map(valid_d_wr, valid_ce3, valid_rd_wr, valid_d_rd, clk);

bus_creator2_hm_tag: bus_creator2 port map(cpu_add_stored(3), cpu_add_stored(2), hm_tag);
hm: hit_miss_detector port map(tb_d_rd, hm_tag, valid_d_rd, hit_miss);

oe_cpu_data: output_enable8 port map(cb_d_rd, cpu_data_oe, cpu_data);

bus_creator6_mem_add: bus_creator6 port map(
    cpu_add_stored(5),
    cpu_add_stored(4),
    cpu_add_stored(3),
    cpu_add_stored(2),
    b0, b0,
    mem_add_out
);
oe_mem_add: output_enable6 port map(mem_add_out, mem_add_oe, mem_add);

end structural;

-- File: basics/buff.vhd
-- Buffer using 2 inverters

library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity buff is
    port(
        input    : in std_logic;
        output   : out std_logic
    );
end buff;

```

```

architecture structural of buff is
    component inverter
        port(
            input    : in std_logic;
            output   : out std_logic
        );
    end component;

    for inverter_0, inverter_1: inverter use entity work.inverter(structural);

    signal x: std_logic;

begin
    inverter_0: inverter port map(input, x);
    inverter_1: inverter port map(x, output);

end structural;

```

```

-- File: basics/bus_creator2.vhd
-- 2 bit bus creator, converts 2 input bits to a single bus

```

```

library STD;
library IEEE;
use IEEE.std_logic_1164.all;

```

```

entity bus_creator2 is
    port(
        input1   : in std_logic;
        input0   : in std_logic;
        output    : out std_logic_vector(1 downto 0)
    );
end bus_creator2;

```

```

architecture structural of bus_creator2 is
    component buff
        port(
            input    : in std_logic;
            output   : out std_logic
        );
    end component;

    for buff_0, buff_1: buff use entity work.buff(structural);

begin

    buff_0: buff port map(input0, output(0));
    buff_1: buff port map(input1, output(1));

end structural;

```

```

-- File: basics/bus_creator6.vhd
-- 6 bit bus creator, converts 6 input lines into a single 6 bit bus

```

```

library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity bus_creator6 is
    port(
        input5  : in std_logic;
        input4  : in std_logic;
        input3  : in std_logic;
        input2  : in std_logic;
        input1  : in std_logic;
        input0  : in std_logic;
        output   : out std_logic_vector(5 downto 0)
    );
end bus_creator6;

architecture structural of bus_creator6 is
    component buff
        port(
            input   : in std_logic;
            output  : out std_logic
        );
    end component;

    for buff_0, buff_1, buff_2, buff_3, buff_4, buff_5: buff use entity work.buff(structural);

begin

    buff_0: buff port map(input0, output(0));
    buff_1: buff port map(input1, output(1));
    buff_2: buff port map(input2, output(2));
    buff_3: buff port map(input3, output(3));
    buff_4: buff port map(input4, output(4));
    buff_5: buff port map(input5, output(5));

end structural;

-- File: basics/comparator2.vhd
-- 2-bit comparator
-- Outputs 1 when inputs are equal

library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity comparator2 is
    port(
        input1  : in std_logic_vector(1 downto 0);
        input2  : in std_logic_vector(1 downto 0);
        output   : out std_logic
    );
end comparator2;

architecture structural of comparator2 is
    component xor2

```

```

        port(
            input1  : in std_logic;
            input2  : in std_logic;
            output  : out std_logic
        );
    end component;

    component nor2
    port(
        input1  : in std_logic;
        input2  : in std_logic;
        output  : out std_logic
    );
    end component;

    for xor2_0, xor2_1: xor2 use entity work.xor2(structural);
    for nor2_0: nor2 use entity work.nor2(structural);

    signal x, y: std_logic;

begin
    xor2_0: xor2 port map(input1(0), input2(0), x);
    xor2_1: xor2 port map(input1(1), input2(1), y);

    nor2_0: nor2 port map(x, y, output);

end structural;

-- File: basics/comparator5s.vhd
-- 5 bit comparator (different types of inputs)
-- outputs 1 when input1 and all equivalent bits of input2 are equal

library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity comparator5s is
    port(
        input1      : in std_logic_vector(4 downto 0);
        input2_0    : in std_logic;
        input2_1    : in std_logic;
        input2_2    : in std_logic;
        input2_3    : in std_logic;
        input2_4    : in std_logic;
        output      : out std_logic
    );
end comparator5s;

architecture structural of comparator5s is
    component xor2
    port(
        input1  : in std_logic;
        input2  : in std_logic;
        output  : out std_logic
    );
    end component;

```

```

component nor2
  port(
    input1  : in std_logic;
    input2  : in std_logic;
    output  : out std_logic
  );
end component;

component or4
  port(
    input1  : in std_logic;
    input2  : in std_logic;
    input3  : in std_logic;
    input4  : in std_logic;
    output  : out std_logic
  );
end component;

for xor2_0, xor2_1, xor2_2, xor2_3, xor2_4: xor2 use entity work.xor2(structural);
for nor2_0: nor2 use entity work.nor2(structural);
for or4_0: or4 use entity work.or4(structural);

signal a,b,c,d,e,f: std_logic;

begin
  xor2_0: xor2 port map(input1(0), input2_0, a);
  xor2_1: xor2 port map(input1(1), input2_1, b);
  xor2_2: xor2 port map(input1(2), input2_2, c);
  xor2_3: xor2 port map(input1(3), input2_3, d);
  xor2_4: xor2 port map(input1(4), input2_4, e);

  or4_0: or4 port map(a, b, c, d, f);

  nor2_0: nor2 port map(f, e, output);

end structural;

-- File: basics/decoder2to4.vhd
library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity decoder2to4 is
  port(
    input0  : in std_logic;
    input1  : in std_logic;
    output0 : out std_logic;
    output1 : out std_logic;
    output2 : out std_logic;
    output3 : out std_logic
  );
end decoder2to4;

architecture structural of decoder2to4 is
  -- components

```



```

component and2
  port(
    input1 : in std_logic;
    input2 : in std_logic;
    output  : out std_logic
  );
end component;

component inverter
  port(
    input  : in std_logic;
    output : out std_logic
  );
end component;

for and2_0, and2_1, and2_2, and2_3: and2 use entity work.and2(structural);
for inv_0, inv_1: inverter use entity work.inverter(structural);

-- optional wires
signal in0n: std_logic;
signal in1n: std_logic;

begin
  inv_0: inverter port map(input0, in0n);
  inv_1: inverter port map(input1, in1n);

  and2_0: and2 port map(in0n, in1n, output0);
  and2_1: and2 port map(input0, in1n, output1);
  and2_2: and2 port map(in0n, input1, output2);
  and2_3: and2 port map(input0, input1, output3);

end structural;

-- File: basics/decoder3to8.vhd
library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity decoder3to8 is
  port(
    en      : in std_logic;
    input0  : in std_logic;
    input1  : in std_logic;
    input2  : in std_logic;
    output0 : out std_logic;
    output1 : out std_logic;
    output2 : out std_logic;
    output3 : out std_logic;
    output4 : out std_logic;
    output5 : out std_logic;
    output6 : out std_logic;
    output7 : out std_logic
  );
end decoder3to8;

architecture structural of decoder3to8 is

```

```

component and3
  port(
    input1 : in std_logic;
    input2 : in std_logic;
    input3 : in std_logic;
    output  : out std_logic
  );
end component;

component and2
  port(
    input1 : in std_logic;
    input2 : in std_logic;
    output  : out std_logic
  );
end component;

component inverter
  port(
    input  : in std_logic;
    output : out std_logic
  );
end component;

for and3_0, and3_1, and3_2, and3_3, and3_4, and3_5, and3_6, and3_7: and3 use entity work.and3(structural);
for and2_0, and2_1, and2_2, and2_3, and2_4, and2_5, and2_6, and2_7: and2 use entity work.and2(structural);
for inv_0, inv_1, inv_2: inverter use entity work.inverter(structural);

signal in0n, in1n, in2n: std_logic;
signal o0, o1, o2, o3, o4, o5, o6, o7: std_logic;

begin

  inv_0: inverter port map(input0, in0n);
  inv_1: inverter port map(input1, in1n);
  inv_2: inverter port map(input2, in2n);

  and3_0: and3 port map(in0n, in1n, in2n, o0);
  and3_1: and3 port map(input0, in1n, in2n, o1);
  and3_2: and3 port map(in0n, input1, in2n, o2);
  and3_3: and3 port map(input0, input1, in2n, o3);
  and3_4: and3 port map(in0n, in1n, input2, o4);
  and3_5: and3 port map(input0, in1n, input2, o5);
  and3_6: and3 port map(in0n, input1, input2, o6);
  and3_7: and3 port map(input0, input1, input2, o7);

  and2_0: and2 port map(o0, en, output0);
  and2_1: and2 port map(o1, en, output1);
  and2_2: and2 port map(o2, en, output2);
  and2_3: and2 port map(o3, en, output3);
  and2_4: and2 port map(o4, en, output4);
  and2_5: and2 port map(o5, en, output5);
  and2_6: and2 port map(o6, en, output6);
  and2_7: and2 port map(o7, en, output7);

end structural;

```

```

-- File: basics/decoder4to16.vhd
library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity decoder4to16 is
    port(
        input      : in std_logic_vector(3 downto 0);
        output0    : out std_logic;
        output1    : out std_logic;
        output2    : out std_logic;
        output3    : out std_logic;
        output4    : out std_logic;
        output5    : out std_logic;
        output6    : out std_logic;
        output7    : out std_logic;
        output8    : out std_logic;
        output9    : out std_logic;
        output10   : out std_logic;
        output11   : out std_logic;
        output12   : out std_logic;
        output13   : out std_logic;
        output14   : out std_logic;
        output15   : out std_logic
    );
end decoder4to16;

architecture structural of decoder4to16 is
    -- components
    component decoder3to8
        port(
            en      : in std_logic;
            input0  : in std_logic;
            input1  : in std_logic;
            input2  : in std_logic;
            output0 : out std_logic;
            output1 : out std_logic;
            output2 : out std_logic;
            output3 : out std_logic;
            output4 : out std_logic;
            output5 : out std_logic;
            output6 : out std_logic;
            output7 : out std_logic
        );
    end component;

    component inverter
        port(
            input   : in std_logic;
            output  : out std_logic
        );
    end component;

    for dec3to8_0, dec3to8_1: decoder3to8 use entity work.decoder3to8(structural);
    for inv_0: inverter use entity work.inverter(structural);

```

```

    signal input3bar: std_logic;

begin

    inv_0: inverter port map(input(3), input3bar);

    dec3to8_0: decoder3to8 port map(input3bar, input(0), input(1), input(2), output0, output1, output2,
    dec3to8_1: decoder3to8 port map(input(3), input(0), input(1), input(2), output8, output9, output10);

end structural;

-- File: basics/dffer4.vhd
-- 4-bit register using dffer

library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity dffer4 is
    port(
        d      : in std_logic_vector(3 downto 0);
        clk    : in std_logic;
        ce     : in std_logic;
        rst    : in std_logic;
        q      : out std_logic_vector(3 downto 0);
        qbar   : out std_logic_vector(3 downto 0)
    );
end dffer4;

architecture structural of dffer4 is
    component dffer
        port(
            d      : in std_logic;
            clk    : in std_logic;
            ce     : in std_logic;
            rst    : in std_logic;
            q      : out std_logic;
            qbar   : out std_logic
        );
    end component;

    for dffer_0, dffer_1, dffer_2, dffer_3
        : dffer use entity work.dffer(structural);

begin
    dffer_0: dffer port map(d(0), clk, ce, rst, q(0), qbar(0));
    dffer_1: dffer port map(d(1), clk, ce, rst, q(1), qbar(1));
    dffer_2: dffer port map(d(2), clk, ce, rst, q(2), qbar(2));
    dffer_3: dffer port map(d(3), clk, ce, rst, q(3), qbar(3));

end structural;

-- File: basics/dffer.vhd
-- Negative edge-triggered DFF with chip enable and synchronous reset

```

```

library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity dffer is
  port(
    d      : in std_logic;
    clk    : in std_logic;
    ce     : in std_logic;
    rst    : in std_logic;
    q      : out std_logic;
    qbar   : out std_logic
  );
end dffer;

architecture structural of dffer is
  component dff
    port(
      d      : in std_logic;
      clk    : in std_logic;
      q      : out std_logic;
      qbar   : out std_logic
    );
  end component;

  component and2
    port(
      input1  : in std_logic;
      input2  : in std_logic;
      output  : out std_logic
    );
  end component;

  component inverter
    port(
      input   : in std_logic;
      output  : out std_logic
    );
  end component;

  component mux2
    port(
      input0  : in std_logic;
      input1  : in std_logic;
      s       : in std_logic;
      output  : out std_logic
    );
  end component;

  component buff
    port(
      input   : in std_logic;
      output  : out std_logic
    );
  end component;

  for dff_0: dff use entity work.dff(structural);

```

```

    for and2_0: and2 use entity work.and2(structural);
    for inverter_0: inverter use entity work.inverter(structural);
    for mux2_0: mux2 use entity work.mux2(structural);
    for buff_0: buff use entity work.buff(structural);

    signal rstn, de, dg, qi: std_logic;

begin
    inverter_0: inverter port map(rst, rstn);

    mux2_0: mux2 port map(qi, d, ce, de);

    and2_0: and2 port map(de, rstn, dg);

    dff_0: dff port map(dg, clk, qi, qbar);

    buff_0: buff port map(qi, q);

end structural;

-- File: basics/dlatch6.vhd
library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity dlatch6 is
    port(
        d      : in std_logic_vector(5 downto 0);
        clk    : in std_logic;
        q      : out std_logic_vector(5 downto 0);
        qbar   : out std_logic_vector(5 downto 0)
    );
end dlatch6;

architecture structural of dlatch6 is
    component Dlatch
        port ( d      : in std_logic;
              clk    : in std_logic;
              q      : out std_logic;
              qbar   : out std_logic);
    end component;

    for dl_0, dl_1, dl_2, dl_3, dl_4, dl_5: Dlatch use entity work.Dlatch(structural);

begin
    dl_0: Dlatch port map(d(0), clk, q(0), qbar(0));
    dl_1: Dlatch port map(d(1), clk, q(1), qbar(1));
    dl_2: Dlatch port map(d(2), clk, q(2), qbar(2));
    dl_3: Dlatch port map(d(3), clk, q(3), qbar(3));
    dl_4: Dlatch port map(d(4), clk, q(4), qbar(4));
    dl_5: Dlatch port map(d(5), clk, q(5), qbar(5));

end structural;

-- File: basics/dlatch8.vhd

```

```

library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity dlatch8 is
  port(
    d      : in std_logic_vector(7 downto 0);
    clk    : in std_logic;
    q      : out std_logic_vector(7 downto 0);
    qbar   : out std_logic_vector(7 downto 0)
  );
end dlatch8;

architecture structural of dlatch8 is
  component Dlatch
    port ( d      : in std_logic;
          clk    : in std_logic;
          q      : out std_logic;
          qbar   : out std_logic);
  end component;

  for dl_0, dl_1, dl_2, dl_3, dl_4, dl_5, dl_6, dl_7: Dlatch use entity work.Dlatch(structural);

begin
  dl_0: Dlatch port map(d(0), clk, q(0), qbar(0));
  dl_1: Dlatch port map(d(1), clk, q(1), qbar(1));
  dl_2: Dlatch port map(d(2), clk, q(2), qbar(2));
  dl_3: Dlatch port map(d(3), clk, q(3), qbar(3));
  dl_4: Dlatch port map(d(4), clk, q(4), qbar(4));
  dl_5: Dlatch port map(d(5), clk, q(5), qbar(5));
  dl_6: Dlatch port map(d(6), clk, q(6), qbar(6));
  dl_7: Dlatch port map(d(7), clk, q(7), qbar(7));

end structural;

-- File: basics/encoder16to4.vhd
library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity encoder16to4 is
  port(
    input0      : in std_logic;
    input1      : in std_logic;
    input2      : in std_logic;
    input3      : in std_logic;
    input4      : in std_logic;
    input5      : in std_logic;
    input6      : in std_logic;
    input7      : in std_logic;
    input8      : in std_logic;
    input9      : in std_logic;
    input10     : in std_logic;
    input11     : in std_logic;
    input12     : in std_logic;
    input13     : in std_logic;
  );

```

```

        input14      : in std_logic;
        input15      : in std_logic;
        output       : out std_logic_vector(3 downto 0)
    );
end encoder16to4;

architecture structural of encoder16to4 is
    component or4
        port(
            input1: in std_logic;
            input2: in std_logic;
            input3: in std_logic;
            input4: in std_logic;
            output: out std_logic
        );
    end component;

    component or2
        port(
            input1: in std_logic;
            input2: in std_logic;
            output: out std_logic
        );
    end component;

    for or4_0, or4_1, or4_2, or4_3, or4_4, or4_5,
        or4_6, or4_7: or4 use entity work.or4(structural);

    for or2_0, or2_1, or2_2, or2_3: or2 use entity work.or2(structural);

    signal a,b,c,d,e,f,g,h: std_logic;

begin
    -- o0 = odds
    or4_0 : or4 port map(input1, input3, input5, input7, a);
    or4_1 : or4 port map(input9, input11, input13, input15, b);
    or2_0 : or2 port map(a,b, output(0));

    -- o1 = 2,3,6,7,10,11,14,15,18,19,22,23,26,27,30,31
    or4_2 : or4 port map(input2, input3, input6, input7, c);
    or4_3 : or4 port map(input10, input11, input14, input15, d);
    or2_1 : or2 port map(c,d, output(1));

    -- o2 = 4-7, 12-15, 20-23, 28-31
    or4_4 : or4 port map(input4, input5, input6, input7, e);
    or4_5 : or4 port map(input12, input13, input14, input15, f);
    or2_2 : or2 port map(e,f, output(2));

    -- o3 = 8-15, 24-31
    or4_6 : or4 port map(input8, input9, input10, input11, g);
    or4_7 : or4 port map(input12, input13, input14, input15, h);
    or2_3 : or2 port map(g,h, output(3));

end structural;

```



```

-- File: basics/mux2.vhd
-- 2-to-1 mux

library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity mux2 is
    port(
        input0  : in std_logic;
        input1  : in std_logic;
        s       : in std_logic;
        output  : out std_logic
    );
end mux2;

architecture structural of mux2 is
    component or2
        port(
            input1  : in std_logic;
            input2  : in std_logic;
            output  : out std_logic
        );
    end component;

    component and2
        port(
            input1  : in std_logic;
            input2  : in std_logic;
            output  : out std_logic
        );
    end component;

    component inverter
        port(
            input    : in std_logic;
            output   : out std_logic
        );
    end component;

    for or2_0: or2 use entity work.or2(structural);
    for and2_0, and2_1: and2 use entity work.and2(structural);
    for inverter_0: inverter use entity work.inverter(structural);

    signal sn, in0g, in1g: std_logic;

begin
    inverter_0: inverter port map(s, sn);

    and2_0: and2 port map(input0, sn, in0g);
    and2_1: and2 port map(input1, s, in1g);

    or2_0: or2 port map(in0g, in1g, output);

end structural;

```

```

-- File: cache/cache_4byte.vhd
-- 4-byte cache row

library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity cache_4byte is
    port(
        d_wr      : in std_logic_vector(7 downto 0);
        ce        : in std_logic;
        rd_wr      : in std_logic;
        -- need decode bits
        a0         : in std_logic;
        a1         : in std_logic;
        d_rd       : out std_logic_vector(7 downto 0);
        clk        : in std_logic
    );
end cache_4byte;

architecture structural of cache_4byte is
    -- components
    component cache_cell8
        port(
            d_wr      : in std_logic_vector(7 downto 0);
            ce        : in std_logic;
            rd_wr      : in std_logic;
            d_rd       : out std_logic_vector(7 downto 0);
            clk        : in std_logic
        );
    end component;

    component decoder2to4
        port(
            input0    : in std_logic;
            input1    : in std_logic;
            output0    : out std_logic;
            output1    : out std_logic;
            output2    : out std_logic;
            output3    : out std_logic
        );
    end component;

    component and2
        port(
            input1    : in std_logic;
            input2    : in std_logic;
            output     : out std_logic
        );
    end component;

    for cell8_0, cell8_1, cell8_2, cell8_3: cache_cell8 use entity work.cache_cell8(structural);
    for decoder: decoder2to4 use entity work.decoder2to4(structural);
    for and2_0, and2_1, and2_2, and2_3: and2 use entity work.and2(structural);

    signal ce0, ce1, ce2, ce3: std_logic;

```

```

    signal ce0g, ce1g, ce2g, ce3g: std_logic;

begin
    decoder: decoder2to4 port map(a0, a1, ce0, ce1, ce2, ce3);
    and2_0: and2 port map(ce, ce0, ce0g);
    and2_1: and2 port map(ce, ce1, ce1g);
    and2_2: and2 port map(ce, ce2, ce2g);
    and2_3: and2 port map(ce, ce3, ce3g);
    cell8_0: cache_cell8 port map(d_wr, ce0g, rd_wr, d_rd, clk);
    cell8_1: cache_cell8 port map(d_wr, ce1g, rd_wr, d_rd, clk);
    cell8_2: cache_cell8 port map(d_wr, ce2g, rd_wr, d_rd, clk);
    cell8_3: cache_cell8 port map(d_wr, ce3g, rd_wr, d_rd, clk);

end structural;

-- File: cache/cache_block.vhd
-- cache block of 4 rows

library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity cache_block is
    port(
        d_wr      : in std_logic_vector(7 downto 0);
        ce        : in std_logic;
        rd_wr     : in std_logic;
        index0    : in std_logic;
        index1    : in std_logic;
        offset0   : in std_logic;
        offset1   : in std_logic;
        d_rd      : out std_logic_vector(7 downto 0);
        clk       : in std_logic
    );
end cache_block;

architecture structural of cache_block is
    -- components
    component cache_4byte
        port(
            d_wr      : in std_logic_vector(7 downto 0);
            ce        : in std_logic;
            rd_wr     : in std_logic;
            a0        : in std_logic;
            a1        : in std_logic;
            d_rd      : out std_logic_vector(7 downto 0);
            clk       : in std_logic
        );
    end component;

    component decoder2to4
        port(
            input0    : in std_logic;
            input1    : in std_logic;

```

```

        output0 : out std_logic;
        output1 : out std_logic;
        output2 : out std_logic;
        output3 : out std_logic
    );
end component;

component and2
    port(
        input1 : in std_logic;
        input2 : in std_logic;
        output  : out std_logic
    );
end component;

for row_0, row_1, row_2, row_3: cache_4byte use entity work.cache_4byte(structural);
for decoder: decoder2to4 use entity work.decoder2to4(structural);
for and2_0, and2_1, and2_2, and2_3: and2 use entity work.and2(structural);

signal ce0, ce1, ce2, ce3: std_logic;

signal ce0g, ce1g, ce2g, ce3g: std_logic;

begin
    decoder: decoder2to4 port map(index0, index1, ce0, ce1, ce2, ce3);
    and2_0: and2 port map(ce, ce0, ce0g);
    and2_1: and2 port map(ce, ce1, ce1g);
    and2_2: and2 port map(ce, ce2, ce2g);
    and2_3: and2 port map(ce, ce3, ce3g);
    row_0: cache_4byte port map(d_wr, ce0g, rd_wr, offset0, offset1, d_rd, clk);
    row_1: cache_4byte port map(d_wr, ce1g, rd_wr, offset0, offset1, d_rd, clk);
    row_2: cache_4byte port map(d_wr, ce2g, rd_wr, offset0, offset1, d_rd, clk);
    row_3: cache_4byte port map(d_wr, ce3g, rd_wr, offset0, offset1, d_rd, clk);

end structural;

-- File: cache/cache_cell1.vhd
-- 1-bit cache cell, using positive edge-triggered dffer

library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity cache_cell1 is
    port(
        d_wr      : in std_logic;
        ce        : in std_logic;
        rd_wr     : in std_logic;
        d_rd      : out std_logic;
        clk       : in std_logic
    );
end cache_cell1;

architecture structural of cache_cell1 is
    component dffer
        port(

```

```

        d      : in std_logic;
        clk    : in std_logic;
        ce     : in std_logic;
        rst    : in std_logic;
        q      : out std_logic;
        qbar   : out std_logic
    );
end component;

component tx
    port(
        sel     : in std_logic;
        selnot  : in std_logic;
        input   : in std_logic;
        output  : out std_logic
    );
end component;

component inverter
    port(
        input   : in std_logic;
        output  : out std_logic
    );
end component;

component cache_decoder
    port(
        ce      : in std_logic;
        rd_wr   : in std_logic;
        we      : out std_logic;
        re      : out std_logic
    );
end component;

component tie_low
    port(
        output: out std_logic
    );
end component;

for dffer_0: dffer use entity work.dffer(structural);
for tx_0: tx use entity work.tx(structural);
for inverter_0, inverter_1: inverter use entity work.inverter(structural);
for cache_decoder_0: cache_decoder use entity work.cache_decoder(structural);
for tie_low_0: tie_low use entity work.tie_low(structural);

signal we, re, re_n, q, b0, clk_n: std_logic;

begin
    tie_low_0: tie_low port map(b0);

    inverter_0: inverter port map(clk, clk_n);

    dffer_0: dffer port map(d_wr, clk_n, we, b0, q, open);

    tx_0: tx port map(re, re_n, q, d_rd);

```

```

    inverter_1: inverter port map(re, re_n);

    cache_decoder_0: cache_decoder port map(ce, rd_wr, we, re);

end structural;

-- File: cache/cache_cell2.vhd
-- 2-bit cache cell

library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity cache_cell2 is
    port(
        d_wr      : in std_logic_vector(1 downto 0);
        ce        : in std_logic;
        rd_wr     : in std_logic;
        d_rd      : out std_logic_vector(1 downto 0);
        clk       : in std_logic
    );
end cache_cell2;

architecture structural of cache_cell2 is
    component cache_cell1
        port(
            d_wr      : in std_logic;
            ce        : in std_logic;
            rd_wr     : in std_logic;
            d_rd      : out std_logic;
            clk       : in std_logic
        );
    end component;

    for cache_cell1_0, cache_cell1_1: cache_cell1 use entity work.cache_cell1(structural);

begin
    cache_cell1_0: cache_cell1 port map(d_wr(0), ce, rd_wr, d_rd(0), clk);
    cache_cell1_1: cache_cell1 port map(d_wr(1), ce, rd_wr, d_rd(1), clk);

end structural;

-- File: cache/cache_cell8.vhd
-- 8-bit cache cell

library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity cache_cell8 is
    port(
        d_wr      : in std_logic_vector(7 downto 0);
        ce        : in std_logic;
        rd_wr     : in std_logic;
        d_rd      : out std_logic_vector(7 downto 0);
    );
end cache_cell8;

```

```

        clk      : in std_logic
    );
end cache_cell8;

architecture structural of cache_cell8 is
    component cache_cell1
        port(
            d_wr    : in std_logic;
            ce      : in std_logic;
            rd_wr   : in std_logic;
            d_rd    : out std_logic;
            clk     : in std_logic
        );
    end component;

    for cache_cell1_0, cache_cell1_1, cache_cell1_2, cache_cell1_3,
        cache_cell1_4, cache_cell1_5, cache_cell1_6, cache_cell1_7
        : cache_cell1 use entity work.cache_cell1(structural);

begin
    cache_cell1_0: cache_cell1 port map(d_wr(0), ce, rd_wr, d_rd(0), clk);
    cache_cell1_1: cache_cell1 port map(d_wr(1), ce, rd_wr, d_rd(1), clk);
    cache_cell1_2: cache_cell1 port map(d_wr(2), ce, rd_wr, d_rd(2), clk);
    cache_cell1_3: cache_cell1 port map(d_wr(3), ce, rd_wr, d_rd(3), clk);
    cache_cell1_4: cache_cell1 port map(d_wr(4), ce, rd_wr, d_rd(4), clk);
    cache_cell1_5: cache_cell1 port map(d_wr(5), ce, rd_wr, d_rd(5), clk);
    cache_cell1_6: cache_cell1 port map(d_wr(6), ce, rd_wr, d_rd(6), clk);
    cache_cell1_7: cache_cell1 port map(d_wr(7), ce, rd_wr, d_rd(7), clk);

end structural;

-- File: cache/cache_decoder.vhd
-- Decoder for cache cell

library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity cache_decoder is
    port(
        ce      : in std_logic;
        rd_wr   : in std_logic;
        we      : out std_logic;
        re      : out std_logic
    );
end cache_decoder;

architecture structural of cache_decoder is
    -- components
    component and2
        port(
            input1 : in std_logic;
            input2 : in std_logic;
            output  : out std_logic
        );

```

```

end component;

component inverter
  port(
    input   : in std_logic;
    output  : out std_logic
  );
end component;

for and2_0, and2_1: and2 use entity work.and2(structural);
for inv_0: inverter use entity work.inverter(structural);

-- ce & rd_wr = re
-- ce & !rd_wr = we
signal x: std_logic;

begin
  inv_0: inverter port map(rd_wr, x);

  and2_0: and2 port map(ce, rd_wr, re);

  and2_1: and2 port map(ce, x, we);

end structural;

-- File: cache/tag_block.vhd
-- 4 rows of 2 bits for tag within the cache

library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity tag_block is
  port(
    d_wr      : in std_logic_vector(1 downto 0);
    ce        : in std_logic;
    rd_wr     : in std_logic;
    index0    : in std_logic;
    index1    : in std_logic;
    d_rd      : out std_logic_vector(1 downto 0);
    clk       : in std_logic
  );
end tag_block;

architecture structural of tag_block is
  component cache_cell2
    port(
      d_wr      : in std_logic_vector(1 downto 0);
      ce        : in std_logic;
      rd_wr     : in std_logic;
      d_rd      : out std_logic_vector(1 downto 0);
      clk       : in std_logic
    );
  end component;

```



```

component decoder2to4
  port(
    input0  : in std_logic;
    input1  : in std_logic;
    output0 : out std_logic;
    output1 : out std_logic;
    output2 : out std_logic;
    output3 : out std_logic
  );
end component;

component and2
  port(
    input1  : in std_logic;
    input2  : in std_logic;
    output  : out std_logic
  );
end component;

for row_0, row_1, row_2, row_3: cache_cell2 use entity work.cache_cell2(structural);
for decoder: decoder2to4 use entity work.decoder2to4(structural);
for and2_0, and2_1, and2_2, and2_3: and2 use entity work.and2(structural);

signal ce0, ce1, ce2, ce3: std_logic;

signal ce0g, ce1g, ce2g, ce3g: std_logic;

begin
  decoder: decoder2to4 port map(index0, index1, ce0, ce1, ce2, ce3);
  and2_0: and2 port map(ce, ce0, ce0g);
  and2_1: and2 port map(ce, ce1, ce1g);
  and2_2: and2 port map(ce, ce2, ce2g);
  and2_3: and2 port map(ce, ce3, ce3g);
  row_0: cache_cell2 port map(d_wr, ce0g, rd_wr, d_rd, clk);
  row_1: cache_cell2 port map(d_wr, ce1g, rd_wr, d_rd, clk);
  row_2: cache_cell2 port map(d_wr, ce2g, rd_wr, d_rd, clk);
  row_3: cache_cell2 port map(d_wr, ce3g, rd_wr, d_rd, clk);

end structural;

-- File: control/hit_miss_detector.vhd
-- Hit miss detector
-- takes the value of valid, and tag from both cache and
-- address to compare

library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity hit_miss_detector is
  port(
    input1  : in std_logic_vector(1 downto 0);
    input2  : in std_logic_vector(1 downto 0);
    valid   : in std_logic;
    output  : out std_logic
  );

```

```

end hit_miss_detector;

architecture structural of hit_miss_detector is
    component and2
        port(
            input1 : in std_logic;
            input2 : in std_logic;
            output  : out std_logic
        );
    end component;

    component comparator2
        port(
            input1 : in std_logic_vector(1 downto 0);
            input2 : in std_logic_vector(1 downto 0);
            output  : out std_logic
        );
    end component;

    for comp2_0: comparator2 use entity work.comparator2(structural);
    for and2_0: and2 use entity work.and2(structural);

    signal x: std_logic;

begin
    -- valid & comparator2(input1, input2) == hit

    comp2_0: comparator2 port map(input1, input2, x);

    and2_0: and2 port map(valid, x, output);

end structural;

-- File: control/output_enable6.vhd
-- Output enable module for C_a and M_d
-- controls when outputs are to be allowed out of the shared in/out pins, as well as memory address passing

library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity output_enable6 is
    port(
        input   : in std_logic_vector(5 downto 0);
        oe      : in std_logic;
        output  : out std_logic_vector(5 downto 0)
    );
end output_enable6;

architecture structural of output_enable6 is
    component tx
        port(
            sel      : in std_logic;
            selnot   : in std_logic;
            input    : in std_logic;
            output   : out std_logic
        );
    end component;

```

```

    );
end component;

component inverter
    port(
        input    : in std_logic;
        output   : out std_logic
    );
end component;

for tx_0, tx_1, tx_2, tx_3, tx_4, tx_5: tx use entity work.tx(structural);
for inv: inverter use entity work.inverter(structural);

signal oe_n: std_logic;

begin
    inv: inverter port map(oe, oe_n);

    tx_0: tx port map(oe, oe_n, input(0), output(0));
    tx_1: tx port map(oe, oe_n, input(1), output(1));
    tx_2: tx port map(oe, oe_n, input(2), output(2));
    tx_3: tx port map(oe, oe_n, input(3), output(3));
    tx_4: tx port map(oe, oe_n, input(4), output(4));
    tx_5: tx port map(oe, oe_n, input(5), output(5));

end structural;

-- File: control/output_enable8.vhd
-- Output enable module for C_a and M_d
-- controls when outputs are to be allowed out of the shared in/out pins, as well as memory address passes

library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity output_enable8 is
    port(
        input    : in std_logic_vector(7 downto 0);
        oe       : in std_logic;
        output    : out std_logic_vector(7 downto 0)
    );
end output_enable8;

architecture structural of output_enable8 is
    component tx
        port(
            sel      : in std_logic;
            selnot   : in std_logic;
            input     : in std_logic;
            output    : out std_logic
        );
    end component;

    component inverter
        port(
            input     : in std_logic;

```

```

        output : out std_logic
    );
end component;

for tx_0, tx_1, tx_2, tx_3, tx_4, tx_5, tx_6, tx_7: tx use entity work.tx(structural);
for inv: inverter use entity work.inverter(structural);

signal oe_n: std_logic;

begin
    inv: inverter port map(oe, oe_n);

    tx_0: tx port map(oe, oe_n, input(0), output(0));
    tx_1: tx port map(oe, oe_n, input(1), output(1));
    tx_2: tx port map(oe, oe_n, input(2), output(2));
    tx_3: tx port map(oe, oe_n, input(3), output(3));
    tx_4: tx port map(oe, oe_n, input(4), output(4));
    tx_5: tx port map(oe, oe_n, input(5), output(5));
    tx_6: tx port map(oe, oe_n, input(6), output(6));
    tx_7: tx port map(oe, oe_n, input(7), output(7));

end structural;

-- File: control/statemachine_notes.txt
--- Pseudocode output equations ---
[brackets] are bit positions of state code
"state" is the decimal value of [3:0]

cpu_busy =
    [3] or is_state04 or is_state06

counter_ce =
    is_state12 or is_state13 or is_state08

counter_rst =
    is_state06 or is_state01

cpu_data_oe =
    is_state05 or is_state07

mem_add_oe =
    is_state12

mem_enable =
    is_state12

cb_d_wr_control =
    is_state08

cb_ce =
    [3] xor [2]

cb_rd_wr =
    [3]' and [2]

cb_offset_control =

```

```

        is_state08

tb_ce =
    is_state04 or is_state08 or is_state14

tb_rd_wr =
    is_state04 or is_state14

valid_ce =
    is_state04 or is_state08 or is_state14

valid_ce_all =
    is_state01

valid_rd_wr =
    is_state04 or is_state14

valid_d_wr =
    is_state08

```

```

-- File: control/statemachine.vhd
-- State machine for cache

```

```

library STD;
library IEEE;
use IEEE.std_logic_1164.all;

```

```

entity statemachine is
    port(
        clk                : in std_logic;

        -- Inputs
        cpu_rd_wrn         : in std_logic;
        cpu_start          : in std_logic;
        cpu_reset          : in std_logic;

        count1             : in std_logic;
        count2             : in std_logic;

        hit_miss           : in std_logic;

        -- Outputs
        cpu_busy           : out std_logic;

        counter_ce         : out std_logic;
        counter_rst        : out std_logic;

        cpu_data_oe        : out std_logic;
        mem_add_oe         : out std_logic;

        mem_enable         : out std_logic;

        cb_d_wr_control    : out std_logic;

        cb_ce              : out std_logic;
        cb_rd_wr           : out std_logic;
    );
end entity statemachine;

```

```

        cb_offset_control    : out std_logic;

        tb_ce                : out std_logic;
        tb_rd_wr             : out std_logic;

        valid_ce             : out std_logic;
        valid_ce_all         : out std_logic;

        valid_rd_wr          : out std_logic;
        valid_d_wr           : out std_logic;
    );
end statemachine;

```

architecture structural of statemachine is

```

    component tie_high
    port(
        output: out std_logic
    );
end component;

    component tie_low
    port(
        output: out std_logic
    );
end component;

    component inverter
    port(
        input   : in std_logic;
        output  : out std_logic
    );
end component;

    component and2
    port(
        input1   : in std_logic;
        input2   : in std_logic;
        output   : out std_logic
    );
end component;

    component and3
    port(
        input1   : in std_logic;
        input2   : in std_logic;
        input3   : in std_logic;
        output   : out std_logic
    );
end component;

    component and4
    port(
        input1   : in std_logic;
        input2   : in std_logic;
        input3   : in std_logic;
        input4   : in std_logic;
    );
end component;

```

```

        output : out std_logic
    );
end component;

component or2
    port(
        input1 : in std_logic;
        input2 : in std_logic;
        output  : out std_logic
    );
end component;

component or3
    port(
        input1 : in std_logic;
        input2 : in std_logic;
        input3 : in std_logic;
        output  : out std_logic
    );
end component;

component or4
    port(
        input1: in std_logic;
        input2: in std_logic;
        input3: in std_logic;
        input4: in std_logic;
        output: out std_logic
    );
end component;

component xor2
    port(
        input1 : in std_logic;
        input2 : in std_logic;
        output  : out std_logic
    );
end component;

component buff
    port(
        input  : in std_logic;
        output : out std_logic
    );
end component;

component dffer4
    port(
        d      : in std_logic_vector(3 downto 0);
        clk    : in std_logic;
        ce     : in std_logic;
        rst    : in std_logic;
        q      : out std_logic_vector(3 downto 0);
        qbar   : out std_logic_vector(3 downto 0)
    );
end component;

```

```

component decoder4to16
  port(
    input      : in std_logic_vector(3 downto 0);
    output0    : out std_logic;
    output1    : out std_logic;
    output2    : out std_logic;
    output3    : out std_logic;
    output4    : out std_logic;
    output5    : out std_logic;
    output6    : out std_logic;
    output7    : out std_logic;
    output8    : out std_logic;
    output9    : out std_logic;
    output10   : out std_logic;
    output11   : out std_logic;
    output12   : out std_logic;
    output13   : out std_logic;
    output14   : out std_logic;
    output15   : out std_logic
  );
end component;

component encoder16to4
  port(
    input0      : in std_logic;
    input1      : in std_logic;
    input2      : in std_logic;
    input3      : in std_logic;
    input4      : in std_logic;
    input5      : in std_logic;
    input6      : in std_logic;
    input7      : in std_logic;
    input8      : in std_logic;
    input9      : in std_logic;
    input10     : in std_logic;
    input11     : in std_logic;
    input12     : in std_logic;
    input13     : in std_logic;
    input14     : in std_logic;
    input15     : in std_logic;
    output      : out std_logic_vector(3 downto 0)
  );
end component;

for tie_high_0: tie_high use entity work.tie_high(structural);

for tie_low_0: tie_low use entity work.tie_low(structural);

for inverter_0, inverter_1, inverter_2, inverter_3, inverter_4,
  inverter_5, inverter_6
  : inverter use entity work.inverter(structural);

for and2_0, and2_1, and2_2, and2_3, and2_4, and2_5, and2_6
  : and2 use entity work.and2(structural);

for and3_0, and3_1, and3_2, and3_3, and3_4, and3_5, and3_6, and3_7,

```



```

    and3_8, and3_9
    : and3 use entity work.and3(structural);

for and4_0, and4_1, and4_2, and4_3: and4 use entity work.and4(structural);

for or2_0, or2_1, or2_2, or2_3, or2_4, or2_5, or2_6, or2_7
    : or2 use entity work.or2(structural);

for or3_0, or3_1, or3_2: or3 use entity work.or3(structural);

for or4_0: or4 use entity work.or4(structural);

for xor2_0: xor2 use entity work.xor2(structural);

for buff_0, buff_1, buff_2, buff_3, buff_4, buff_5, buff_6, buff_7,
    buff_8, buff_9, buff_10
    : buff use entity work.buff(structural);

for dffer4_0: dffer4 use entity work.dffer4(structural);

for decoder4to16_0: decoder4to16 use entity work.decoder4to16(structural);

for encoder16to4_0: encoder16to4 use entity work.encoder16to4(structural);


-- Analog 1 and 0
signal b1, b0: std_logic;

-- Current state and next state
signal state, nextstate: std_logic_vector(3 downto 0);

-- Intermediate signals
signal s3n, is_state_04_14, is_state_04_08_14: std_logic;

signal cpu_rd_wrn_n, cpu_start_n, cpu_reset_n, count1_n, count2_n, hit_miss_n: std_logic;

signal s00, s01, s02, s03, s04, s05, s06, s07, s08, s09, s10, s11, s12,
    s13, s14
    : std_logic;

signal is_state00, is_state01, is_state04, is_state05, is_state06,
    is_state07, is_state08, is_state09, is_state12, is_state13,
    is_state14, is_state15
    : std_logic;

signal next00, next01, next04, next05, next06, next07, next08, next09,
    next12, next13, next14, next15
    : std_logic;

begin
    tie_high_0: tie_high port map(b1);
    tie_low_0: tie_low port map(b0);

    decoder4to16_0: decoder4to16 port map(
        state,
        is_state00, is_state01, open, open,
        is_state04, is_state05, is_state06, is_state07,

```

```

        is_state08, is_state09, open, open,
        is_state12, is_state13, is_state14, is_state15
    );

encoder16to4_0: encoder16to4 port map(
    next00, next01, b0, b0,
    next04, next05, next06, next07,
    next08, next09, b0, b0,
    next12, next13, next14, next15,
    nextstate
);

-- ----- Transition to next state and store -----

dffer4_0: dffer4 port map(nextstate, clk, b1, b0, state, open);

-- ----- Output logic -----
-- Intermediate signals
inverter_0: inverter port map(state(3), s3n);
or2_0: or2 port map(is_state04, is_state14, is_state_04_14);
or2_1: or2 port map(is_state_04_14, is_state08, is_state_04_08_14);

-- cpu_busy
or3_0: or3 port map(state(3), is_state04, is_state06, cpu_busy);

-- counter_ce
or3_1: or3 port map(is_state12, is_state13, is_state08, counter_ce);

-- counter_rst
or2_2: or2 port map(is_state06, is_state01, counter_rst);

-- cpu_data_oe
or2_3: or2 port map(is_state05, is_state07, cpu_data_oe);

-- mem_add_oe
buff_0: buff port map(is_state12, mem_add_oe);

-- mem_enable
buff_1: buff port map(is_state12, mem_enable);

-- cb_d_wr_control
buff_2: buff port map(is_state08, cb_d_wr_control);

-- cb_ce
xor2_0: xor2 port map(state(3), state(2), cb_ce);

-- cb_rd_wr
and2_0: and2 port map(s3n, state(2), cb_rd_wr);

-- cb_offset_control
buff_3: buff port map(is_state08, cb_offset_control);

-- tb_ce
buff_4: buff port map(is_state_04_08_14, tb_ce);

```

```

-- tb_rd_wr
buff_5: buff port map(is_state_04_14, tb_rd_wr);

-- valid_ce
buff_6: buff port map(is_state_04_08_14, valid_ce);

-- valid_ce_all
buff_7: buff port map(is_state01, valid_ce_all);

-- valid_rd_wr
buff_8: buff port map(is_state_04_14, valid_rd_wr);

-- valid_d_wr
buff_9: buff port map(is_state08, valid_d_wr);

-- ----- Next state logic -----
-- Intermediate signals
inverter_1: inverter port map(cpu_rd_wrn, cpu_rd_wrn_n);
inverter_2: inverter port map(cpu_start, cpu_start_n);
inverter_3: inverter port map(cpu_reset, cpu_reset_n);
inverter_4: inverter port map(count1, count1_n);
inverter_5: inverter port map(count2, count2_n);
inverter_6: inverter port map(hit_miss, hit_miss_n);

-- -> idle
and3_0: and3 port map(is_state00, cpu_start_n, cpu_reset_n, s00); -- idle -> idle
and2_1: and2 port map(is_state07, cpu_reset_n, s01); -- rd_miss_send -> idle
and2_2: and2 port map(is_state05, cpu_reset_n, s02); -- rd_hit -> idle
and2_3: and2 port map(is_state15, cpu_reset_n, s03); -- wr_miss -> idle
and2_4: and2 port map(is_state09, cpu_reset_n, s04); -- wr_hit -> idle
and3_1: and3 port map(is_state01, cpu_start_n, cpu_reset_n, s05); -- reset -> idle
or4_0: or4 port map(s00, s01, s02, s03, s06);
or3_2: or3 port map(s06, s04, s05, next00);

-- -> rd_init
and4_0: and4 port map(is_state00, cpu_rd_wrn, cpu_start, cpu_reset_n, s07); -- idle -
> rd_init
and4_1: and4 port map(is_state01, cpu_rd_wrn, cpu_start, cpu_reset_n, s08); -- reset -
> rd_init
or2_4: or2 port map(s07, s08, next04);

-- rd_init -> rd_miss_mem_enable
and3_2: and3 port map(is_state04, cpu_reset_n, hit_miss_n, next12);

-- -> rd_miss_mem_wait
and2_5: and2 port map(is_state12, cpu_reset_n, s09); -- rd_miss_mem_enable -
> rd_miss_mem_wait
and3_3: and3 port map(is_state13, cpu_reset_n, count1_n, s10); -- rd_miss_mem_wait -
> rd_miss_mem_wait
or2_5: or2 port map(s09, s10, next13);

-- -> rd_miss_wr
and3_4: and3 port map(is_state13, cpu_reset_n, count1, s11); -- rd_miss_mem_wait -
> rd_miss_wr
and3_5: and3 port map(is_state08, cpu_reset_n, count2_n, s12); -- rd_miss_wr -
> rd_miss_wr

```

```

or2_6: or2 port map(s11, s12, next08);

-- rd_miss_wr -> rd_miss_rd
and3_6: and3 port map(is_state08, cpu_reset_n, count2, next06);

-- rd_miss_rd -> rd_miss_send
and2_6: and2 port map(is_state06, cpu_reset_n, next07);

-- rd_init -> rd_hit
and3_7: and3 port map(is_state04, cpu_reset_n, hit_miss, next05);

-- -> wr_init
and4_2: and4 port map(is_state00, cpu_rd_wrn_n, cpu_start, cpu_reset_n, s13); --
idle -> wr_init
and4_3: and4 port map(is_state01, cpu_rd_wrn_n, cpu_start, cpu_reset_n, s14); --
reset -> wr_init
or2_7: or2 port map(s13, s14, next14);

-- wr_init -> wr_miss
and3_8: and3 port map(is_state14, cpu_reset_n, hit_miss_n, next15);

-- wr_init -> wr_hit
and3_9: and3 port map(is_state14, cpu_reset_n, hit_miss, next09);

-- any state -> reset
buff_10: buff port map(cpu_reset, next01);

```

```
end structural;
```

```

-- File: control/valid_ce_gen.vhd
-- Generates ce for the 4 cache cells storing valid bits

```

```

library STD;
library IEEE;
use IEEE.std_logic_1164.all;

```

```

entity valid_ce_gen is
  port(
    index0:      in std_logic;
    index1:      in std_logic;
    valid_ce:    in std_logic;
    valid_ce_all: in std_logic;
    valid_ce0:   out std_logic;
    valid_ce1:   out std_logic;
    valid_ce2:   out std_logic;
    valid_ce3:   out std_logic
  );
end valid_ce_gen;

```

```

architecture structural of valid_ce_gen is
  component decoder2to4
    port(
      input0 : in std_logic;
      input1 : in std_logic;
      output0 : out std_logic;
      output1 : out std_logic;

```

```

        output2 : out std_logic;
        output3 : out std_logic
    );
end component;

component and2
    port(
        input1 : in std_logic;
        input2 : in std_logic;
        output  : out std_logic
    );
end component;

component or2
    port(
        input1 : in std_logic;
        input2 : in std_logic;
        output  : out std_logic
    );
end component;

for decoder: decoder2to4 use entity work.decoder2to4(structural);
for and2_0, and2_1, and2_2, and2_3: and2 use entity work.and2(structural);
for or2_0, or2_1, or2_2, or2_3: or2 use entity work.or2(structural);

signal vce0, vce1, vce2, vce3, vce0g, vce1g, vce2g, vce3g: std_logic;

begin
    -- Determine which ce would be selected normally
    decoder: decoder2to4 port map(index0, index1, vce0, vce1, vce2, vce3);

    -- Gate with valid_ce
    and2_0: and2 port map(vce0, valid_ce, vce0g);
    and2_1: and2 port map(vce1, valid_ce, vce1g);
    and2_2: and2 port map(vce2, valid_ce, vce2g);
    and2_3: and2 port map(vce3, valid_ce, vce3g);

    -- Override with 1 if valid_ce_all is 1
    or2_0: or2 port map(vce0g, valid_ce_all, valid_ce0);
    or2_1: or2 port map(vce1g, valid_ce_all, valid_ce1);
    or2_2: or2 port map(vce2g, valid_ce_all, valid_ce2);
    or2_3: or2 port map(vce3g, valid_ce_all, valid_ce3);

end structural;

-- File: counter/adder1.vhd
-- 1-bit full adder

library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity adder1 is
    port(
        input1 : in std_logic;
        input2 : in std_logic;

```

```

        carryin    : in std_logic;
        sum        : out std_logic;
        carryout   : out std_logic
    );
end adder1;

architecture structural of adder1 is
    component xor2
        port(
            input1   : in std_logic;
            input2   : in std_logic;
            output    : out std_logic
        );
    end component;

    component and2
        port(
            input1   : in std_logic;
            input2   : in std_logic;
            output    : out std_logic
        );
    end component;

    component or3
        port(
            input1   : in std_logic;
            input2   : in std_logic;
            input3   : in std_logic;
            output    : out std_logic
        );
    end component;

    for xor2_1, xor2_2: xor2 use entity work.xor2(structural);
    for and2_1, and2_2, and2_3: and2 use entity work.and2(structural);
    for or3_1: or3 use entity work.or3(structural);

    signal temp1, temp2, temp3, temp4: std_logic;

begin
    xor2_1: xor2 port map (input1, input2, temp1);
    xor2_2: xor2 port map (carryin, temp1, sum);

    and2_1: and2 port map (input1, input2, temp2);
    and2_2: and2 port map (input1, carryin, temp3);
    and2_3: and2 port map (input2, carryin, temp4);

    or3_1: or3 port map (temp2, temp3, temp4, carryout);

end structural;

-- File: counter/adder5.vhd
-- 5-bit full adder

library STD;
library IEEE;
use IEEE.std_logic_1164.all;

```

```

entity adder5 is
    port(
        input1      : in std_logic_vector(4 downto 0);
        input2      : in std_logic_vector(4 downto 0);
        carryin     : in std_logic;
        sum         : out std_logic_vector(4 downto 0);
        carryout    : out std_logic
    );
end adder5;

architecture structural of adder5 is
    component adder1
        port(
            input1      : in std_logic;
            input2      : in std_logic;
            carryin     : in std_logic;
            sum         : out std_logic;
            carryout    : out std_logic
        );
    end component;

    for adder1_0, adder1_1, adder1_2, adder1_3, adder1_4: adder1 use entity work.adder1(structural);

    signal ctemp: std_logic_vector(3 downto 0);

begin
    adder1_0: adder1 port map (input1(0), input2(0), carryin, sum(0), ctemp(0));
    adder1_1: adder1 port map (input1(1), input2(1), ctemp(0), sum(1), ctemp(1));
    adder1_2: adder1 port map (input1(2), input2(2), ctemp(1), sum(2), ctemp(2));
    adder1_3: adder1 port map (input1(3), input2(3), ctemp(2), sum(3), ctemp(3));
    adder1_4: adder1 port map (input1(4), input2(4), ctemp(3), sum(4), carryout);

end structural;

-- File: counter/buff5.vhd
-- 5-bit buffer

library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity buff5 is
    port(
        input   : in std_logic_vector(4 downto 0);
        output  : out std_logic_vector(4 downto 0)
    );
end buff5;

architecture structural of buff5 is
    component buff
        port(
            input   : in std_logic;
            output  : out std_logic
        );
    end component;
end structural;

```

```

    for buff_0, buff_1, buff_2, buff_3, buff_4: buff use entity work.buff(structural);

begin
    buff_0: buff port map(input(0), output(0));
    buff_1: buff port map(input(1), output(1));
    buff_2: buff port map(input(2), output(2));
    buff_3: buff port map(input(3), output(3));
    buff_4: buff port map(input(4), output(4));

end structural;

-- File: counter/counter5.vhd
-- Negative edge-triggered 5-bit up-counter

library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity counter5 is
    port(
        clk : in std_logic;
        ce  : in std_logic;
        rst : in std_logic;
        q   : out std_logic_vector(4 downto 0)
    );
end counter5;

architecture structural of counter5 is
    component dffer5
        port(
            d       : in std_logic_vector(4 downto 0);
            clk     : in std_logic;
            ce      : in std_logic;
            rst     : in std_logic;
            q       : out std_logic_vector(4 downto 0);
            qbar    : out std_logic_vector(4 downto 0)
        );
    end component;

    component adder5
        port(
            input1   : in std_logic_vector(4 downto 0);
            input2   : in std_logic_vector(4 downto 0);
            carryin  : in std_logic;
            sum      : out std_logic_vector(4 downto 0);
            carryout : out std_logic
        );
    end component;

    component buff
        port(
            input  : in std_logic;
            output : out std_logic
        );
    end component;

```



```

component buff5
    port(
        input    : in std_logic_vector(4 downto 0);
        output   : out std_logic_vector(4 downto 0)
    );
end component;

component tie_high
    port(
        output: out std_logic
    );
end component;

component tie_low
    port(
        output: out std_logic
    );
end component;

for dffer5_0: dffer5 use entity work.dffer5(structural);
for adder5_0: adder5 use entity work.adder5(structural);
for buff_0, buff_1, buff_2, buff_3, buff_4: buff use entity work.buff(structural);
for buff5_0: buff5 use entity work.buff5(structural);
for tie_high_0: tie_high use entity work.tie_high(structural);
for tie_low_0: tie_low use entity work.tie_low(structural);

signal inc, d, qi: std_logic_vector(4 downto 0);
signal one, zero: std_logic;

begin
    tie_high_0: tie_high port map(one);
    tie_low_0: tie_low port map(zero);

    -- Generate 5-bit number with value 1
    buff_0: buff port map(one, inc(0));
    buff_1: buff port map(zero, inc(1));
    buff_2: buff port map(zero, inc(2));
    buff_3: buff port map(zero, inc(3));
    buff_4: buff port map(zero, inc(4));

    adder5_0: adder5 port map(qi, inc, zero, d, open);

    dffer5_0: dffer5 port map(d, clk, ce, rst, qi, open);

    buff5_0: buff5 port map(qi, q);

end structural;

-- File: counter/dffer5.vhd
-- 5-bit register using dffer

library STD;
library IEEE;
use IEEE.std_logic_1164.all;

```

```

entity dffer5 is
  port(
    d      : in std_logic_vector(4 downto 0);
    clk    : in std_logic;
    ce     : in std_logic;
    rst    : in std_logic;
    q      : out std_logic_vector(4 downto 0);
    qbar   : out std_logic_vector(4 downto 0)
  );
end dffer5;

architecture structural of dffer5 is
  component dffer
    port(
      d      : in std_logic;
      clk    : in std_logic;
      ce     : in std_logic;
      rst    : in std_logic;
      q      : out std_logic;
      qbar   : out std_logic
    );
  end component;

  for dffer_0, dffer_1, dffer_2, dffer_3, dffer_4
    : dffer use entity work.dffer(structural);

begin
  dffer_0: dffer port map(d(0), clk, ce, rst, q(0), qbar(0));
  dffer_1: dffer port map(d(1), clk, ce, rst, q(1), qbar(1));
  dffer_2: dffer port map(d(2), clk, ce, rst, q(2), qbar(2));
  dffer_3: dffer port map(d(3), clk, ce, rst, q(3), qbar(3));
  dffer_4: dffer port map(d(4), clk, ce, rst, q(4), qbar(4));

end structural;

-- File: primitives/and2.vhd
--
-- Entity: and2
-- Architecture : structural
-- Author: cpatel2
-- Created On: 11/11/2003
--
library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity and2 is

  port (
    input1  : in  std_logic;
    input2  : in  std_logic;
    output  : out std_logic);
end and2;

architecture structural of and2 is

```

```

begin

    output <= input2 and input1;

end structural;

-- File: primitives/and3.vhd
library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity and3 is

    port (
        input1    : in  std_logic;
        input2    : in  std_logic;
        input3    : in  std_logic;
        output     : out std_logic);
end and3;

architecture structural of and3 is

begin

    output <= input1 and input2 and input3;

end structural;

-- File: primitives/and4.vhd
library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity and4 is

    port (
        input1    : in  std_logic;
        input2    : in  std_logic;
        input3    : in  std_logic;
        input4    : in  std_logic;
        output     : out std_logic);
end and4;

architecture structural of and4 is

begin

    output <= input1 and input2 and input3 and input4;

end structural;

-- File: primitives/dff.vhd
--
-- Entity: negative edge triggered D flip-flop (dff)

```

```

-- Architecture : structural
-- Author:
--

library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity dff is
  port ( d   : in  std_logic;
        clk : in  std_logic;
        q    : out std_logic;
        qbar : out std_logic);
end dff;

architecture structural of dff is

begin

  output: process

  begin
    wait until ( clk'EVENT and clk = '0' );
    q <= d;
    qbar <= not d ;
  end process output;

end structural;

-- File: primitives/Dlatch.vhd
-- Entity: positive level triggered D latch
-- Architecture : structural
-- Author:
--

library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity Dlatch is
  port ( d   : in  std_logic;
        clk : in  std_logic;
        q    : out std_logic;
        qbar : out std_logic);
end Dlatch;

architecture structural of Dlatch is

begin
  output: process (clk)
  begin
    if(clk = '1') then
      q <= d;
    end if;
  end process;
end structural;

```

```

        qbar <= not d;
    end if;
end process output;

end structural;

-- File: primitives/inverter.vhd
--
-- Entity: inverter
-- Architecture: structural
-- Author: cpatel2
-- Created On: 2022-09-16
--
library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity inverter is

    port (
        input    : in  std_logic;
        output    : out std_logic);
end inverter;

architecture structural of inverter is

begin

    output <= not (input);

end structural;

-- File: primitives/nor2.vhd
library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity nor2 is
    port(
        input1 : in  std_logic;
        input2 : in  std_logic;
        output  : out std_logic
    );
end nor2;

architecture structural of nor2 is
begin
    output <= input1 nor input2;

end structural;

-- File: primitives/or2.vhd
library STD;
library IEEE;

```

```

use IEEE.std_logic_1164.all;

entity or2 is
    port(
        input1 : in std_logic;
        input2 : in std_logic;
        output  : out std_logic
    );
end or2;

architecture structural of or2 is
begin
    output <= input1 or input2;

end structural;

-- File: primitives/or3.vhd
library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity or3 is
    port(
        input1 : in std_logic;
        input2 : in std_logic;
        input3 : in std_logic;
        output  : out std_logic
    );
end or3;

architecture structural of or3 is
begin
    output <= input1 or input2 or input3;

end structural;

-- File: primitives/or4.vhd
--
-- Entity: or4
-- Architecture: structural
-- Author: Daniel Cleaver
-- Created On: 2022-09-16
--
library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity or4 is
    port(
        input1: in std_logic;
        input2: in std_logic;
        input3: in std_logic;
        input4: in std_logic;
        output: out std_logic
    );

```

```

end or4;

architecture structural of or4 is

begin

    output <= input1 or input2 or input3 or input4;

end structural;

```

```

-- File: primitives/tie_high.vhd
--
-- Entity: tie_high
-- Architecture: structural
-- Author: Daniel Cleaver
-- Created On: 2022-10-22
--
library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity tie_high is
    port(
        output: out std_logic
    );
end tie_high;

architecture structural of tie_high is

begin

    output <= '1';

end structural;

```

```

-- File: primitives/tie_low.vhd
--
-- Entity: tie_low
-- Architecture: structural
-- Author: Daniel Cleaver
-- Created On: 2022-10-22
--
library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity tie_low is
    port(
        output: out std_logic
    );
end tie_low;

architecture structural of tie_low is

begin

```

```

        output <= '0';
end structural;

-- File: primitives/tx.vhd
-- Entity: tx -- transmission gate
-- Architecture : structural
-- Author:
--

library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity tx is
    port ( sel    : in std_logic;
          selnot: in std_logic;
          input  : in std_logic;
          output: out std_logic);
end tx;

architecture structural of tx is

begin

    txprocess: process (sel, selnot, input)
    begin
        if (sel = '1' and selnot = '0') then
            output <= input;
        else
            output <= 'Z';
        end if;
    end process txprocess;

end structural;

-- File: primitives/xor2.vhd
--
-- Entity: xor2
-- Architecture : structural
-- Author: cpatel2
-- Created On: 11/11/2003
--

library STD;
library IEEE;
use IEEE.std_logic_1164.all;

entity xor2 is

    port (
        input1    : in  std_logic;
        input2    : in  std_logic;
        output     : out std_logic);
end xor2;

```



```
architecture structural of xor2 is
begin
    output <= input2 xor input1;
end structural;
```

Appendix 2: Testbench and Input/Output File

The input and output text files are the same as the ones provided, but are shown below.

Testbench

```
-- Entity: chip_test
-- Architecture : test
-- Author: cpatel2
-- Created On: 11/01/05
--

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_textio.all;
use IEEE.std_logic_arith.all;
use STD.textio.all;

entity chip_test is

end chip_test;

architecture test of chip_test is

    component chip
        port (
            cpu_add      : in  std_logic_vector(5 downto 0);
            cpu_data      : inout std_logic_vector(7 downto 0);
            cpu_rd_wrn    : in  std_logic;
            start         : in  std_logic;
            clk           : in  std_logic;
            reset         : in  std_logic;
            mem_data      : in  std_logic_vector(7 downto 0);
            Vdd           : in  std_logic;
            Gnd           : in  std_logic;
            busy          : out std_logic;
            mem_en        : out std_logic;
            mem_add       : out std_logic_vector(5 downto 0));
    end component;

    for c1 : chip use entity work.chip(structural);

    signal Vdd, Gnd: std_logic;
    signal cpu_data, mem_data: std_logic_vector(7 downto 0);
    signal cpu_add, mem_add: std_logic_vector(5 downto 0);
    signal cpu_rd_wrn, reset, clk, start, clock, busy, mem_en: std_logic;

    signal clk_count: integer:=0;

    procedure print_output is
        variable out_line: line;

    begin
        write (out_line, string' (" Clock: "));
        write (out_line, clk_count);
```

```

write (out_line, string'(" Start: "));
write (out_line, start);
write (out_line, string'(" Cpu Read/Write: "));
write (out_line, cpu_rd_wrn);
write (out_line, string'(" Reset: "));
write (out_line, reset);
writeline(output, out_line);

write (out_line, string' (" CPU address: "));
write (out_line, cpu_add);
write (out_line, string'(" CPU data: "));
write (out_line, cpu_data);
writeline(output, out_line);

write (out_line, string'(" Memory data: "));
write (out_line, mem_data);
writeline(output, out_line);
writeline(output, out_line);

write (out_line, string'(" Busy: "));
write (out_line, busy);
write (out_line, string'(" Memory Enable: "));
write (out_line, mem_en);
writeline(output, out_line);

write (out_line, string'(" Memory Address: "));
write (out_line, mem_add);
writeline(output, out_line);

write (out_line, string'(" -----"));
writeline(output, out_line);

end print_output;

begin

Vdd <= '1';
Gnd <= '0';
clk <= clock;

c1 : chip port map (cpu_add, cpu_data, cpu_rd_wrn, start, clk, reset, mem_data, Vdd, Gnd, busy, mem_en);

clking : process
begin
    clock<= '1', '0' after 5 ns;
    wait for 10 ns;
end process clking;

io_process: process

    -- Vivado: change "text is in" to "text open read_mode is"
    file infile : text is in "/afs/umbc.edu/users/d/d/dl63/home/cmpe413/proj/cmpe413-
proj/testbenches/example_test1/chip_in.txt";
    variable out_line: line;

```

```

variable buf: line;
variable value: std_logic_vector(7 downto 0);
variable value0: std_logic_vector(5 downto 0);
variable value1: std_logic;

begin

while not (endfile(infile)) loop

    wait until rising_edge(clock);
    print_output;

    readline(infile, buf);
    read(buf, value0);
    cpu_add <= value0;

    readline(infile, buf);
    read(buf, value);
    cpu_data <= value;

    readline(infile, buf);
    read(buf, value1);
    cpu_rd_wrn <= value1;

    readline(infile, buf);
    read(buf, value1);
    start <= value1;

    readline(infile, buf);
    read(buf, value1);
    reset <= value1;

    wait until falling_edge(clock);

    readline(infile, buf);
    read(buf, value);
    mem_data <= value;

    clk_count <= clk_count+1;

    print_output;

end loop;
wait;

-- Vivado: uncomment this
-- std.env.stop;

end process io_process;

end test;

```

Input text file

ZZZZZZ
ZZZZZZZZ
Z
0
1
ZZZZZZZZ
ZZZZZZ
ZZZZZZZZ
Z
0
1
ZZZZZZZZ
000000
ZZZZZZZZ
1
1
0
ZZZZZZZZ
ZZZZZZ
ZZZZZZZZ
Z
0
0
ZZZZZZZZ
ZZZZZZ
ZZZZZZZZ
Z
0
0
ZZZZZZZZ
ZZZZZZ
ZZZZZZZZ
Z
0
0
ZZZZZZZZ
ZZZZZZ
ZZZZZZZZ
Z
0
0
ZZZZZZZZ
ZZZZZZ
ZZZZZZZZ
Z
0
0
00000000
ZZZZZZ
ZZZZZZZZ
Z
0
0
00000000
ZZZZZZ
ZZZZZZZZ
Z
0
0
00000001
ZZZZZZ
ZZZZZZZZ
Z
0
0
00000001
ZZZZZZ
ZZZZZZZZ
Z
0
0
00000010
ZZZZZZ
ZZZZZZZZ
Z
0
0
00000010
ZZZZZZ
ZZZZZZZZ
Z
0
0
00000011
ZZZZZZ
ZZZZZZZZ
Z
0

0
00000011
ZZZZZZ
ZZZZZZZZ
Z
0
0
ZZZZZZZZ
ZZZZZZ
ZZZZZZZZ
Z
0
0
ZZZZZZZZ
ZZZZZZ
ZZZZZZZZ
Z
0
0
ZZZZZZZZ
000011
11111111
0
1
0
ZZZZZZZZ
ZZZZZZ
ZZZZZZZZ
Z
0
0
ZZZZZZZZ
ZZZZZZ
ZZZZZZZZ
Z
0
0
ZZZZZZZZ
ZZZZZZ
ZZZZZZZZ
Z
0
0
ZZZZZZZZ
000011
ZZZZZZZZ
1
1
0
ZZZZZZZZ
ZZZZZZ
ZZZZZZZZ
Z
0
0
ZZZZZZZZ
ZZZZZZ

ZZZZZZZZ
Z
0
0
ZZZZZZZZ
111111
10101010
0
1
0
ZZZZZZZZ
ZZZZZZ
ZZZZZZZZ
Z
0
0
ZZZZZZZZ
ZZZZZZ
ZZZZZZZZ
Z
0
0
ZZZZZZZZ
ZZZZZZ
ZZZZZZZZ
Z
0
0
ZZZZZZZZ
ZZZZZZ
ZZZZZZZZ
Z
0
0
ZZZZZZZZ
ZZZZZZ
ZZZZZZZZ
Z
0
0
ZZZZZZZZ
ZZZZZZ
ZZZZZZZZ
Z
0
0
ZZZZZZZZ

Output text file

```
ncsim: 15.20-s035: (c) Copyright 1995-2017 Cadence Design Systems, Inc.  
T00L:   ncsim   15.20-s035: Started on Nov 22, 2022 at 16:03:13 EST  
ncsim
```

```
-input testbenches/example_test1/run.ncsim  
-messages  
-cdslib /afs/umbc.edu/users/d/d/d163/home/cmpe413/cadence/cds.lib  
-hdlvar /afs/umbc.edu/users/d/d/d163/home/cmpe413/cadence/hdl.var  
chip_test
```

```
Loading snapshot vhdl.chip_test:test ..... Done
```

```
ncsim> run 360 ns
```

```
Clock: 0 Start: U Cpu Read/Write: U Reset: U  
CPU address: UUUUUUU CPU data: UUUUUUUUU  
Memory data: UUUUUUUUU
```

```
Busy: U Memory Enable: U  
Memory Address: ZZZZZZ
```

```
-----  
Clock: 0 Start: 0 Cpu Read/Write: Z Reset: 1  
CPU address: ZZZZZZ CPU data: ZZZZZZZZ  
Memory data: UUUUUUUUU
```

```
Busy: U Memory Enable: U  
Memory Address: ZZZZZZ
```

```
-----  
Clock: 1 Start: 0 Cpu Read/Write: Z Reset: 1  
CPU address: ZZZZZZ CPU data: ZZZZZZZZ  
Memory data: ZZZZZZZZ
```

```
Busy: 0 Memory Enable: 0  
Memory Address: ZZZZZZ
```

```
-----  
Clock: 1 Start: 0 Cpu Read/Write: Z Reset: 1  
CPU address: ZZZZZZ CPU data: ZZZZZZZZ  
Memory data: ZZZZZZZZ
```

```
Busy: 0 Memory Enable: 0  
Memory Address: ZZZZZZ
```

```
-----  
Clock: 2 Start: 0 Cpu Read/Write: Z Reset: 1  
CPU address: ZZZZZZ CPU data: ZZZZZZZZ  
Memory data: ZZZZZZZZ
```

```
Busy: 0 Memory Enable: 0  
Memory Address: ZZZZZZ
```

```
-----  
Clock: 2 Start: 1 Cpu Read/Write: 1 Reset: 0  
CPU address: 000000 CPU data: ZZZZZZZZ  
Memory data: ZZZZZZZZ
```

```
Busy: 0 Memory Enable: 0  
Memory Address: ZZZZZZ
```

```
-----  
Clock: 3 Start: 1 Cpu Read/Write: 1 Reset: 0  
CPU address: 000000 CPU data: ZZZZZZZZ
```

Memory data: ZZZZZZZZ

Busy: 1 Memory Enable: 0

Memory Address: ZZZZZZ

Clock: 3 Start: 0 Cpu Read/Write: Z Reset: 0

CPU address: ZZZZZZ CPU data: ZZZZZZZZ

Memory data: ZZZZZZZZ

Busy: 1 Memory Enable: 0

Memory Address: ZZZZZZ

Clock: 4 Start: 0 Cpu Read/Write: Z Reset: 0

CPU address: ZZZZZZ CPU data: ZZZZZZZZ

Memory data: ZZZZZZZZ

Busy: 1 Memory Enable: 1

Memory Address: 000000

Clock: 4 Start: 0 Cpu Read/Write: Z Reset: 0

CPU address: ZZZZZZ CPU data: ZZZZZZZZ

Memory data: ZZZZZZZZ

Busy: 1 Memory Enable: 1

Memory Address: 000000

Clock: 5 Start: 0 Cpu Read/Write: Z Reset: 0

CPU address: ZZZZZZ CPU data: ZZZZZZZZ

Memory data: ZZZZZZZZ

Busy: 1 Memory Enable: 0

Memory Address: ZZZZZZ

Clock: 5 Start: 0 Cpu Read/Write: Z Reset: 0

CPU address: ZZZZZZ CPU data: ZZZZZZZZ

Memory data: ZZZZZZZZ

Busy: 1 Memory Enable: 0

Memory Address: ZZZZZZ

Clock: 6 Start: 0 Cpu Read/Write: Z Reset: 0

CPU address: ZZZZZZ CPU data: ZZZZZZZZ

Memory data: ZZZZZZZZ

Busy: 1 Memory Enable: 0

Memory Address: ZZZZZZ

Clock: 6 Start: 0 Cpu Read/Write: Z Reset: 0

CPU address: ZZZZZZ CPU data: ZZZZZZZZ

Memory data: ZZZZZZZZ

Busy: 1 Memory Enable: 0

Memory Address: ZZZZZZ

Clock: 7 Start: 0 Cpu Read/Write: Z Reset: 0

CPU address: ZZZZZZ CPU data: ZZZZZZZZ

Memory data: ZZZZZZZZ

```

Busy: 1 Memory Enable: 0
Memory Address: ZZZZZZ
-----
Clock: 7 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: ZZZZZZZZ

Busy: 1 Memory Enable: 0
Memory Address: ZZZZZZ
-----
Clock: 8 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: ZZZZZZZZ

Busy: 1 Memory Enable: 0
Memory Address: ZZZZZZ
-----
Clock: 8 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: ZZZZZZZZ

Busy: 1 Memory Enable: 0
Memory Address: ZZZZZZ
-----
Clock: 9 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: ZZZZZZZZ

Busy: 1 Memory Enable: 0
Memory Address: ZZZZZZ
-----
Clock: 9 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: ZZZZZZZZ

Busy: 1 Memory Enable: 0
Memory Address: ZZZZZZ
-----
Clock: 10 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: ZZZZZZZZ

Busy: 1 Memory Enable: 0
Memory Address: ZZZZZZ
-----
Clock: 10 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: ZZZZZZZZ

Busy: 1 Memory Enable: 0
Memory Address: ZZZZZZ
-----
Clock: 11 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: ZZZZZZZZ

```

```

Busy: 1 Memory Enable: 0
Memory Address: ZZZZZZ
-----
Clock: 11 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: ZZZZZZZZ

Busy: 1 Memory Enable: 0
Memory Address: ZZZZZZ
-----
Clock: 12 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: 00100000

Busy: 1 Memory Enable: 0
Memory Address: ZZZZZZ
-----
Clock: 12 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: 00100000

Busy: 1 Memory Enable: 0
Memory Address: ZZZZZZ
-----
Clock: 13 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: 00100000

Busy: 1 Memory Enable: 0
Memory Address: ZZZZZZ
-----
Clock: 13 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: 00100000

Busy: 1 Memory Enable: 0
Memory Address: ZZZZZZ
-----
Clock: 14 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: 11000001

Busy: 1 Memory Enable: 0
Memory Address: ZZZZZZ
-----
Clock: 14 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: 11000001

Busy: 1 Memory Enable: 0
Memory Address: ZZZZZZ
-----
Clock: 15 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: 11000001

Busy: 1 Memory Enable: 0

```

```

Memory Address: ZZZZZZ
-----
Clock: 15 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: 11000001

Busy: 1 Memory Enable: 0
Memory Address: ZZZZZZ
-----
Clock: 16 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: 10000010

Busy: 1 Memory Enable: 0
Memory Address: ZZZZZZ
-----
Clock: 16 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: 10000010

Busy: 1 Memory Enable: 0
Memory Address: ZZZZZZ
-----
Clock: 17 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: 10000010

Busy: 1 Memory Enable: 0
Memory Address: ZZZZZZ
-----
Clock: 17 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: 10000010

Busy: 1 Memory Enable: 0
Memory Address: ZZZZZZ
-----
Clock: 18 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: 00000011

Busy: 1 Memory Enable: 0
Memory Address: ZZZZZZ
-----
Clock: 18 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: 00000011

Busy: 1 Memory Enable: 0
Memory Address: ZZZZZZ
-----
Clock: 19 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: 00000011

Busy: 1 Memory Enable: 0
Memory Address: ZZZZZZ

```

Clock: 19 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: 00000011

Busy: 1 Memory Enable: 0
Memory Address: ZZZZZZ

Clock: 20 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: ZZZZZZZZ

Busy: 1 Memory Enable: 0
Memory Address: ZZZZZZ

Clock: 20 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: ZZZZZZZZ

Busy: 1 Memory Enable: 0
Memory Address: ZZZZZZ

Clock: 21 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: 00100000
Memory data: ZZZZZZZZ

Busy: 0 Memory Enable: 0
Memory Address: ZZZZZZ

Clock: 21 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: 00100000
Memory data: ZZZZZZZZ

Busy: 0 Memory Enable: 0
Memory Address: ZZZZZZ

Clock: 22 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: ZZZZZZZZ

Busy: 0 Memory Enable: 0
Memory Address: ZZZZZZ

Clock: 22 Start: 1 Cpu Read/Write: 0 Reset: 0
CPU address: 000011 CPU data: 11111111
Memory data: ZZZZZZZZ

Busy: 0 Memory Enable: 0
Memory Address: ZZZZZZ

Clock: 23 Start: 1 Cpu Read/Write: 0 Reset: 0
CPU address: 000011 CPU data: 11111111
Memory data: ZZZZZZZZ

Busy: 1 Memory Enable: 0
Memory Address: ZZZZZZ

Clock: 23 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: ZZZZZZZZ

Busy: 1 Memory Enable: 0
Memory Address: ZZZZZZ

Clock: 24 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: ZZZZZZZZ

Busy: 1 Memory Enable: 0
Memory Address: ZZZZZZ

Clock: 24 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: ZZZZZZZZ

Busy: 1 Memory Enable: 0
Memory Address: ZZZZZZ

Clock: 25 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: ZZZZZZZZ

Busy: 0 Memory Enable: 0
Memory Address: ZZZZZZ

Clock: 25 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: ZZZZZZZZ

Busy: 0 Memory Enable: 0
Memory Address: ZZZZZZ

Clock: 26 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: ZZZZZZZZ

Busy: 0 Memory Enable: 0
Memory Address: ZZZZZZ

Clock: 26 Start: 1 Cpu Read/Write: 1 Reset: 0
CPU address: 000011 CPU data: ZZZZZZZZ
Memory data: ZZZZZZZZ

Busy: 0 Memory Enable: 0
Memory Address: ZZZZZZ

Clock: 27 Start: 1 Cpu Read/Write: 1 Reset: 0
CPU address: 000011 CPU data: ZZZZZZZZ
Memory data: ZZZZZZZZ

Busy: 1 Memory Enable: 0
Memory Address: ZZZZZZ

Clock: 27 Start: 0 Cpu Read/Write: Z Reset: 0

CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: ZZZZZZZZ

Busy: 1 Memory Enable: 0
Memory Address: ZZZZZZ

Clock: 28 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: 11111111
Memory data: ZZZZZZZZ

Busy: 0 Memory Enable: 0
Memory Address: ZZZZZZ

Clock: 28 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: 11111111
Memory data: ZZZZZZZZ

Busy: 0 Memory Enable: 0
Memory Address: ZZZZZZ

Clock: 29 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: ZZZZZZZZ

Busy: 0 Memory Enable: 0
Memory Address: ZZZZZZ

Clock: 29 Start: 1 Cpu Read/Write: 0 Reset: 0
CPU address: 111111 CPU data: 10101010
Memory data: ZZZZZZZZ

Busy: 0 Memory Enable: 0
Memory Address: ZZZZZZ

Clock: 30 Start: 1 Cpu Read/Write: 0 Reset: 0
CPU address: 111111 CPU data: 10101010
Memory data: ZZZZZZZZ

Busy: 1 Memory Enable: 0
Memory Address: ZZZZZZ

Clock: 30 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: ZZZZZZZZ

Busy: 1 Memory Enable: 0
Memory Address: ZZZZZZ

Clock: 31 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: ZZZZZZZZ

Busy: 1 Memory Enable: 0
Memory Address: ZZZZZZ

Clock: 31 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ


```

Memory data: ZZZZZZZZ

Busy: 1 Memory Enable: 0
Memory Address: ZZZZZZ
-----
Clock: 32 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: ZZZZZZZZ

Busy: 0 Memory Enable: 0
Memory Address: ZZZZZZ
-----
Clock: 32 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: ZZZZZZZZ

Busy: 0 Memory Enable: 0
Memory Address: ZZZZZZ
-----
Clock: 33 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: ZZZZZZZZ

Busy: 0 Memory Enable: 0
Memory Address: ZZZZZZ
-----
Clock: 33 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: ZZZZZZZZ

Busy: 0 Memory Enable: 0
Memory Address: ZZZZZZ
-----
Clock: 34 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: ZZZZZZZZ

Busy: 0 Memory Enable: 0
Memory Address: ZZZZZZ
-----
Clock: 34 Start: 0 Cpu Read/Write: Z Reset: 0
CPU address: ZZZZZZ CPU data: ZZZZZZZZ
Memory data: ZZZZZZZZ

Busy: 0 Memory Enable: 0
Memory Address: ZZZZZZ
-----
Ran until 360 NS + 0
ncsim> exit
T00L: ncsim 15.20-s035: Exiting on Nov 22, 2022 at 16:03:14 EST (total: 00:00:01)

```